

CS2022 PROJECT 1- DATAPATH DESIGN


PART A

Aniket Agarwal 17317437

RESULTS OF TEST BENCHES


Register

 The register is given a new value after every 5ns. It works as expected for each edge on a given rising clock signal where the load is high.




Decoder 3_to_8 16 bit

 The test bench cycles through each given combination, causing each given output pin to turn high via the register selection.




Multiplexer 8_to_1 16 bit

 This multiplexer cycles through all given combinations of s1, s2 and s3, thus allowing z to cycle through the inputs in1 to in8 as the output pin.




Multiplexer 2_to_1 16 bit

 The multiplexer cycles through a series of changes via s between 0 and 1. The output of the multiplexer switches between the given outputs for $in1$ and $in2$.




Final VHDL Code

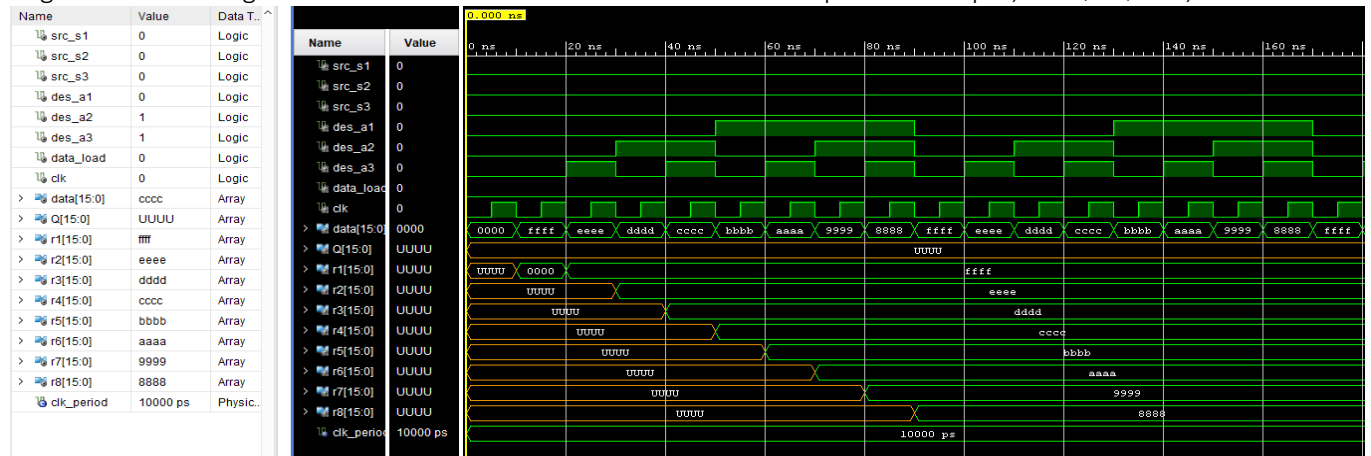Register simulation given different hexadecimal value for each subsequent data input, i.e. $R_i \leftarrow X_i$ $i = 1; 8$



The register $r1$ is loaded with values from the input data from the test bench. The value is then transferred from one given register to the incremented register, $r2$; i.e. from $r1$ to $r2$, $r2$ to $r3$... $r7$ to $r8$. As each load is cycled through the data inputs, the transfer of data cycling between each register is passed on until the input is reset to $0x0000$ after the first input time, which shows that the values stem from the registers, and not from the data input itself sequentially, i.e. $R_i \leftarrow R_j$ $i; j = 0; 7$

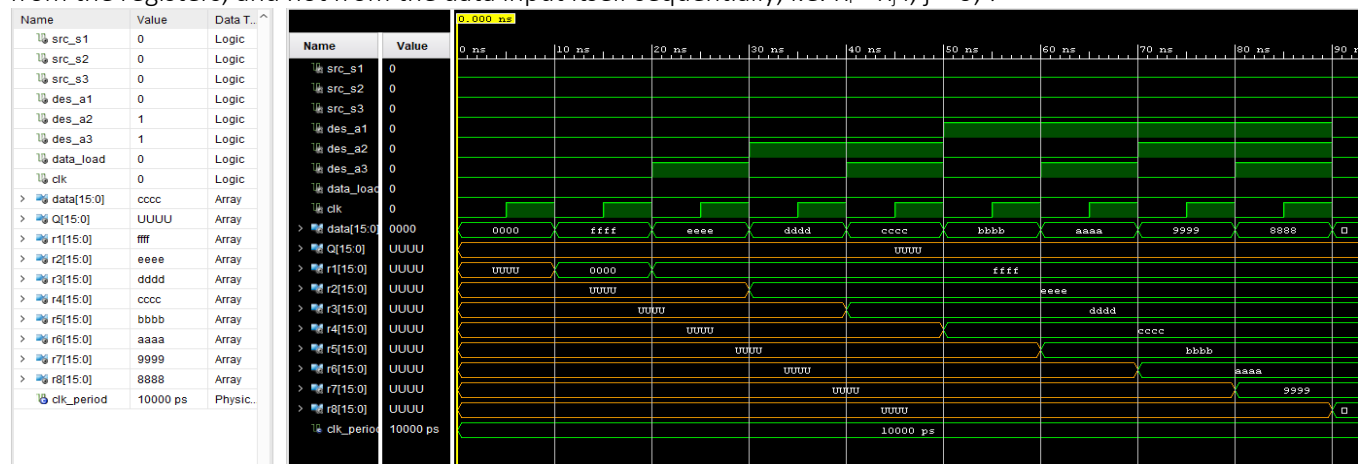

VHDL Components Source Codes

Register

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity reg is
    Port(
        D : in STD_LOGIC_VECTOR(15 downto 0);
        load, clk : in STD_LOGIC;
        Q : out STD_LOGIC_VECTOR(15 downto 0)
    );
end reg;

architecture Behavioral of reg is
begin
    process(clk)
    begin
        if(rising_edge(clk)) then
            if(load = '1') then
                Q <= D after 5ns;
            end if;
        end if;
    end process;
end Behavioral;
```

Decoder 3_to_8 16 bit

library IEEE;

use ieee.std_logic_1164.all;

entity decoder is

port(A1, A2, A3: in std_logic;

D1, D2, D3, D4, D5, D6, D7, D8: out std_logic);

end decoder;

architecture Behavioral of decoder is

begin

D1<=((not A1) and (not A2) and (not A3)) after 5ns ;

D2<=((not A1) and (not A2) and (A3)) after 5ns ;

D3<=((not A1) and (A2) and (not A3)) after 5ns ;

D4<=((not A1) and (A2) and (A3)) after 5ns ;

D5<=((A1) and (not A2) and (not A3)) after 5ns ;

D6<=((A1) and (not A2) and (A3)) after 5ns ;

D7<=((A1) and (A2) and (not A3)) after 5ns ;

D8<=((A1) and (A2) and (A3)) after 5ns ;

end Behavioral;

Multiplexer 8_to_1 16 bit

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity multiplexer is

Port (s1, s2, s3 : in STD_LOGIC;

in1, in2, in3, in4, in5, in6, in7, in8 : in STD_LOGIC_VECTOR (15 downto 0);

z : out STD_LOGIC_VECTOR (15 downto 0));

end multiplexer;

architecture Behavioral of multiplexer is

begin

z <= in1 after 5ns when s1 = '0' and s2 = '0' and s3 = '0' else

in2 after 5ns when s1 = '0' and s2 = '0' and s3 = '1' else

in3 after 5ns when s1 = '0' and s2 = '1' and s3 = '0' else

in4 after 5ns when s1 = '0' and s2 = '1' and s3 = '1' else

in5 after 5ns when s1 = '1' and s2 = '0' and s3 = '0' else

in6 after 5ns when s1 = '1' and s2 = '0' and s3 = '1' else

in7 after 5ns when s1 = '1' and s2 = '1' and s3 = '0' else

in8 after 5ns when s1 = '1' and s2 = '1' and s3 = '1' else

x"0000" after 5ns;

end Behavioral;

Multiplexer 2_to_1 16 bit

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity mux is

Port(

s : in STD_LOGIC;

in1, in2 : in STD_LOGIC_VECTOR(15 downto 0);

z : out STD_LOGIC_VECTOR(15 downto 0)

);

end mux;

architecture Behavioral of mux is

begin

z <= in1 after 5ns when s = '0' else

in2 after 5ns when s = '1' else

x"0000" after 5ns;

end Behavioral;

Final VHDL code

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity register_final is

    Port(

        src_s1, src_s2, src_s3    : in STD_LOGIC;

        des_a1, des_a2, des_a3    : in STD_LOGIC;

        data_load, clk : in STD_LOGIC;

        data      : in STD_LOGIC_VECTOR(15 downto 0);

        Q         : out STD_LOGIC_VECTOR(15 downto 0);

        r1, r2, r3, r4, r5, r6, r7, r8 : out STD_LOGIC_VECTOR(15 downto 0)

    );

end register_final;

architecture Behavioral of register_final is

    Component reg

        Port(

            load, clk      : in    STD_LOGIC;

            D              : in    STD_LOGIC_VECTOR(15 downto 0);

            Q              : out STD_LOGIC_VECTOR(15 downto 0)

        );

    End Component;

    Component decoder

        Port(

            a1, a2, a3 : in STD_LOGIC;

            D1, D2, D3, D4, D5, D6, D7, D8 : out STD_LOGIC

        );

    End Component;

    Component mux

        Port(

            in1, in2 : in STD_LOGIC_VECTOR(15 downto 0);

            s : in STD_LOGIC;
```

```

                                z : out STD_LOGIC_VECTOR(15 downto 0)

                                );

End Component;

Component multiplexer
Port(
    in1, in2, in3, in4, in5, in6, in7, in8 : in STD_LOGIC_VECTOR(15 downto 0);
    s1, s2, s3 : STD_LOGIC;
    z : out STD_LOGIC_VECTOR(15 downto 0)
);

End Component;

signal load_r1, load_r2, load_r3, load_r4, load_r5, load_r6, load_r7, load_r8 : STD_LOGIC;
signal q_r1, q_r2, q_r3, q_r4, q_r5, q_r6, q_r7, q_r8 : STD_LOGIC_VECTOR(15 downto 0);
signal data_src_mux_out, src_r : STD_LOGIC_VECTOR(15 downto 0);

begin

reg1 : reg PORT MAP(
                                load =>          load_r1,
                                clk  =>          clk,
                                D    =>          data_src_mux_out,
                                Q    =>          q_r1);

reg2 : reg PORT MAP(
    load =>  load_r2,
    clk  =>  clk,
    D    =>  data_src_mux_out,
    Q    =>  q_r2
);

reg3 : reg PORT MAP(
    load =>  load_r3,
    clk  =>  clk,
    D    =>  data_src_mux_out,
    Q    =>  q_r3
);

```



```

reg4 : reg PORT MAP(
    load  => load_r4,
    clk   => clk,
    D     => data_src_mux_out,
    Q     => q_r4
);

```

```

reg5 : reg PORT MAP(
    load  => load_r5,
    clk   => clk,
    D     => data_src_mux_out,
    Q     => q_r5
);

```

```

reg6 : reg PORT MAP(
    load  => load_r6,
    clk   => clk,
    D     => data_src_mux_out,
    Q     => q_r6
);

```

```

reg7 : reg PORT MAP(
    load  => load_r7,
    clk   => clk,
    D     => data_src_mux_out,
    Q     => q_r7 );

```

```

reg8 : reg PORT MAP(
    load  => load_r8,
    clk   => clk,
    D     => data_src_mux_out,
    Q     => q_r8
);

```

```

decoder_3_8 : decoder PORT MAP(
    a1      => des_a1,

```

```

a2    =>    des_a2,
a3    =>    des_a3,
D1    =>    load_r1,
D2    =>    load_r2,
D3    =>    load_r3,
D4    =>    load_r4,
D5    =>    load_r5,
D6    =>    load_r6,
D7    =>    load_r7,
D8    =>    load_r8

```

```

);

```

```

mux_2_16 : mux PORT MAP(

```

```

in1    =>    data,
in2    =>    src_r,
s      =>    data_load,
z      =>    data_src_mux_out

```

```

);

```

```

mux_8_16 : multiplexer PORT MAP(

```

```

in1    =>    q_r1,
in2    =>    q_r2,
in3    =>    q_r3,
in4    =>    q_r4,
in5    =>    q_r5,
in6    =>    q_r6,
in7    =>    q_r7,
in8    =>    q_r8,
s1     =>    src_s1,
s2     =>    src_s2,
s3     =>    src_s3,
z      =>    src_r

```

```

);

```

r1 <= q_r1;

r2 <= q_r2;

r3 <= q_r3;

r4 <= q_r4;

r5 <= q_r5;


r6 <= q_r6;

r7 <= q_r7;

r8 <= q_r8;

end Behavioral;

Schematics for the circuit

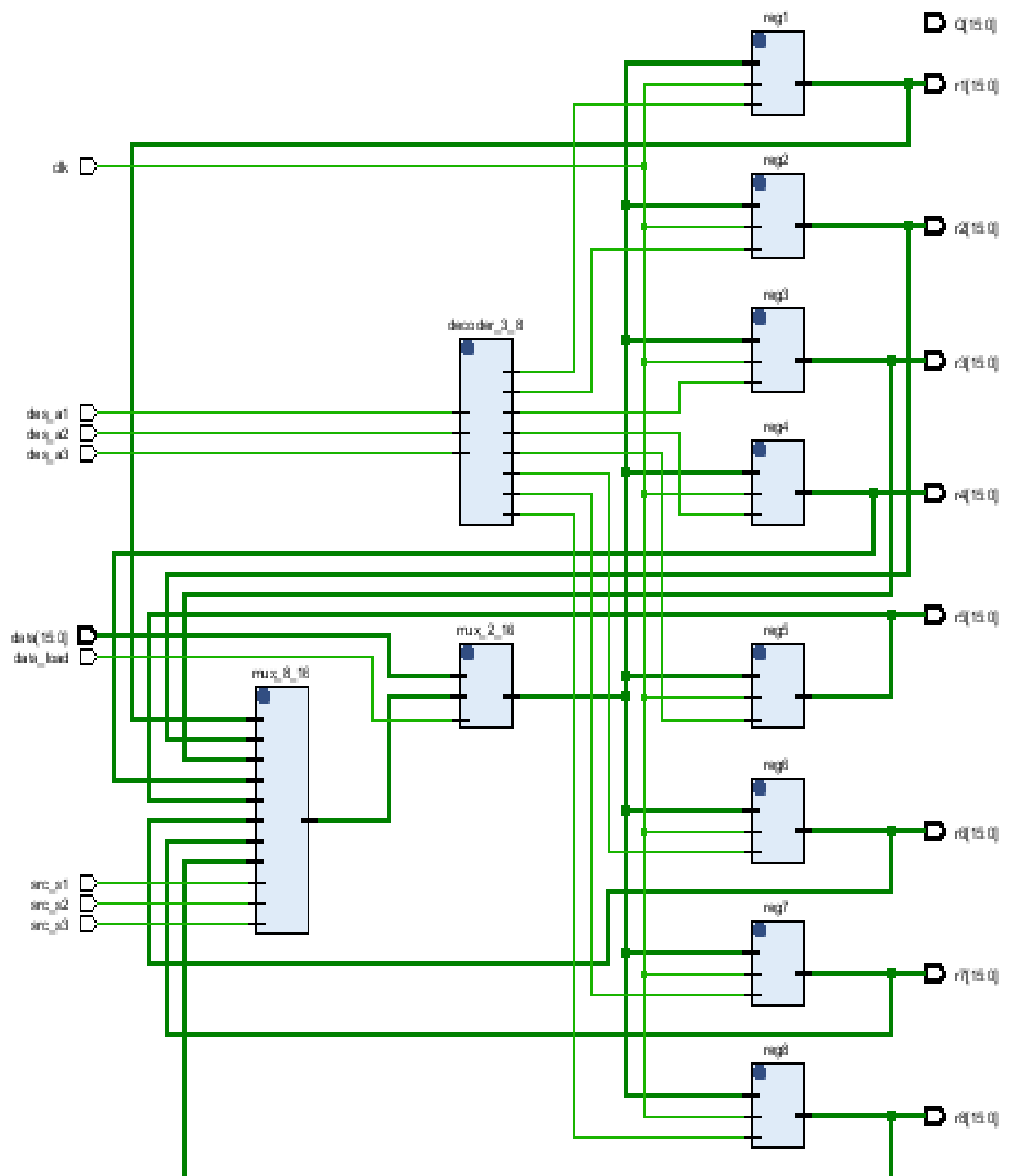

Component Test Benches

Register

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity register_final is
```

```
    Port(
```

```
        src_s1, src_s2, src_s3    : in STD_LOGIC;
```

```
        des_a1, des_a2, des_a3    : in STD_LOGIC;
```

```
        data_load, clk : in STD_LOGIC;
```

```
        data      : in STD_LOGIC_VECTOR(15 downto 0);
```

```
        Q      : out STD_LOGIC_VECTOR(15 downto 0);
```

```
        r1, r2, r3, r4, r5, r6, r7, r8 : out STD_LOGIC_VECTOR(15 downto 0)
```

```
    );
```

```
end register_final;
```

```
architecture Behavioral of register_final is
```

```
    Component reg
```

```
        Port(
```

```
            load, clk      : in      STD_LOGIC;
```

```
            D              : in STD_LOGIC_VECTOR(15 downto 0);
```

```
            Q              : out STD_LOGIC_VECTOR(15 downto 0)
```

```
        );
```

```
    End Component;
```

```
    Component decoder
```

```
        Port(
```

```
            a1, a2, a3 : in STD_LOGIC;
```

```
            D1, D2, D3, D4, D5, D6, D7, D8 : out STD_LOGIC
```

```
        );
```

```
    End Component;
```

```
    Component mux
```

```
        Port(
```

```
            in1, in2 : in STD_LOGIC_VECTOR(15 downto 0);
```

```

        s : in STD_LOGIC;

        z : out STD_LOGIC_VECTOR(15 downto 0)

    );

End Component;

Component multiplexer

    Port(

        in1, in2, in3, in4, in5, in6, in7, in8 : in STD_LOGIC_VECTOR(15 downto 0);

        s1, s2, s3 : STD_LOGIC;

        z : out STD_LOGIC_VECTOR(15 downto 0)

    );

End Component;

signal load_r1, load_r2, load_r3, load_r4, load_r5, load_r6, load_r7, load_r8 : STD_LOGIC;
signal q_r1, q_r2, q_r3, q_r4, q_r5, q_r6, q_r7, q_r8 : STD_LOGIC_VECTOR(15 downto 0);
signal data_src_mux_out, src_r : STD_LOGIC_VECTOR(15 downto 0);
begin

    reg1 : reg PORT MAP(

        load  =>    load_r1,

        clk   =>    clk,

        D     =>    data_src_mux_out,

        Q     =>    q_r1

    );

    reg2 : reg PORT MAP(

        load  =>    load_r2,

        clk   =>    clk,

        D     =>    data_src_mux_out,

        Q     =>    q_r2

    );

    reg3 : reg PORT MAP(

        load  =>    load_r3,

        clk   =>    clk,

        D     =>    data_src_mux_out,

        Q     =>    q_r3

    );

```

```

reg4 : reg PORT MAP(
    load  => load_r4,
    clk   => clk,
    D     => data_src_mux_out,
    Q     => q_r4 );

reg5 : reg PORT MAP(
    load  => load_r5,
    clk   => clk,
    D     => data_src_mux_out,
    Q     => q_r5 );

reg6 : reg PORT MAP(
    load  => load_r6,
    clk   => clk,
    D     => data_src_mux_out,
    Q     => q_r6 );

reg7 : reg PORT MAP(
    load  => load_r7,
    clk   => clk,
    D     => data_src_mux_out,
    Q     => q_r7 );

reg8 : reg PORT MAP(
    load  => load_r8,
    clk   => clk,
    D     => data_src_mux_out,
    Q     => q_r8 );

decoder_3_8 : decoder PORT MAP(
    a1     => des_a1,
    a2     => des_a2,
    a3     => des_a3,
    D1     => load_r1,
    D2     => load_r2,

```

```

        D3    =>    load_r3,
        D4    =>    load_r4,
        D5    =>    load_r5,
        D6    =>    load_r6,
        D7    =>    load_r7,
        D8    =>    load_r8 );

mux_2_16 : mux PORT MAP(
        in1    =>    data,
        in2    =>    src_r,
        s      =>    data_load,
        z      =>    data_src_mux_out);

mux_8_16 : multiplexer PORT MAP(
        in1    =>    q_r1,
        in2    =>    q_r2,
        in3    =>    q_r3,
        in4    =>    q_r4,
        in5    =>    q_r5,
        in6    =>    q_r6,
        in7    =>    q_r7,
        in8    =>    q_r8,
        s1     =>    src_s1,
        s2     =>    src_s2,
        s3     =>    src_s3,
        z      =>    src_r    );

r1 <= q_r1;r2 <= q_r2;  r3 <= q_r3;r4 <= q_r4;  r5 <= q_r5;r6 <= q_r6;  r7 <= q_r7;r8 <= q_r8;

end Behavioral;
```


Decoder 3_to_8 16 bit

```
library IEEE;

use IEEE.Std_logic_1164.all;

use IEEE.Numeric_Std.all;

entity decoder_tb is
end;

architecture behavior of decoder_tb is
    component decoder
    port(A1, A2, A3: in std_logic;
        D1, D2, D3, D4, D5, D6, D7, D8: out std_logic);
    end component;

    signal A1, A2, A3: std_logic;
    signal D1, D2, D3, D4, D5, D6, D7, D8: std_logic;

begin
    uut: decoder port map ( A1 => A1, A2 => A2, A3 => A3,
        D1 => D1, D2 => D2, D3 => D3, D4 => D4, D5 => D5, D6 => D6, D7 => D7, D8 => D8
    );

    stimulus: process
    begin
        wait for 10ns; A1 <= '0'; A2 <= '0'; A3 <= '0';
        wait for 10ns; A1 <= '0'; A2 <= '0'; A3 <= '1';
        wait for 10ns; A1 <= '0'; A2 <= '1'; A3 <= '0';
        wait for 10ns; A1 <= '0'; A2 <= '1'; A3 <= '1';
        wait for 10ns; A1 <= '1'; A2 <= '0'; A3 <= '0';
        wait for 10ns; A1 <= '1'; A2 <= '0'; A3 <= '1';
        wait for 10ns; A1 <= '1'; A2 <= '1'; A3 <= '0';
        wait for 10ns; A1 <= '1'; A2 <= '1'; A3 <= '1';

        wait;
    end process;

end;
```

Multiplexer 8_to_1 16 bit

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

ENTITY multiplexer_tb IS

END multiplexer_tb;

ARCHITECTURE behavior OF multiplexer_tb IS

COMPONENT multiplexer

PORT(

    s1: IN  std_logic;

    s2: IN  std_logic;

    s3: IN  std_logic;

    in1 : IN  std_logic_vector(15 downto 0);

    in2 : IN  std_logic_vector(15 downto 0);

    in3 : IN  std_logic_vector(15 downto 0);

    in4 : IN  std_logic_vector(15 downto 0);

    in5 : IN  std_logic_vector(15 downto 0);

    in6 : IN  std_logic_vector(15 downto 0);

    in7 : IN  std_logic_vector(15 downto 0);

    in8 : IN  std_logic_vector(15 downto 0);

    z : OUT std_logic_vector(15 downto 0)

);

END COMPONENT;

signal s1 : std_logic := '0';

signal s2 : std_logic := '0';

signal s3 : std_logic := '0';

signal in1 : std_logic_vector(15 downto 0) := (others => '0');

signal in2 : std_logic_vector(15 downto 0) := (others => '0');

signal in3 : std_logic_vector(15 downto 0) := (others => '0');

signal in4 : std_logic_vector(15 downto 0) := (others => '0');

signal in5 : std_logic_vector(15 downto 0) := (others => '0');

signal in6 : std_logic_vector(15 downto 0) := (others => '0');
```

```

signal in7 : std_logic_vector(15 downto 0) := (others => '0');
signal in8 : std_logic_vector(15 downto 0) := (others => '0');
signal z : std_logic_vector(15 downto 0);

BEGIN

    uut: multiplexer PORT MAP (
        s1 => s1,s2 => s2,s3 => s3,
        in1 => in1,in2 => in2,in3 => in3,in4 => in4,in5 => in5,in6 => in6,in7 => in7,in8 => in8,
        z => z
    );

stim_proc: process
begin

    in1 <= x"FFFF";
    in2 <= x"EEEE";
    in3 <= x"DDDD";
    in4 <= x"CCCC";
    in5 <= x"BBBB";
    in6 <= x"AAAA";
    in7 <= x"9999";
    in8 <= x"8888";

    wait for 10ns;  s1 <= '1';s2 <= '0';s3 <= '0';
    wait for 10ns;  s1 <= '0';s2 <= '1';s3 <= '0';
    wait for 10ns;  s1 <= '1';s2 <= '1';s3 <= '0';
    wait for 10ns;  s1 <= '0';s2 <= '0';s3 <= '1';
    wait for 10ns;  s1 <= '1';s2 <= '0';s3 <= '1';
    wait for 10ns;  s1 <= '0';s2 <= '1';s3 <= '1';
    wait for 10ns;  s1 <= '1';s2 <= '1';s3 <= '1';

    end process;

END;

```

Multiplexer 2_to_1 16 bit

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

ENTITY mux_tb IS

END mux_tb;

ARCHITECTURE behavior OF mux_tb IS

COMPONENT mux

PORT(

    in1 : IN std_logic_vector(15 downto 0);

    in2 : IN std_logic_vector(15 downto 0);

    s : IN std_logic;

    z : OUT std_logic_vector(15 downto 0)

);

END COMPONENT;

signal in1 : std_logic_vector(15 downto 0) := (others => '0');
signal in2 : std_logic_vector(15 downto 0) := (others => '0');
signal s : std_logic := '0';
signal z : std_logic_vector(15 downto 0);

BEGIN

mux_2_16: mux PORT MAP (

    in1 => in1,    in2 => in2,

    s => s,    z => z    );

stim_proc: process

begin

    wait for 10ns; in1 <= x"FFFF"; in2 <= x"AAAA";

    wait for 10ns; s <= '1';

    wait for 10ns; s <= '0';

    wait for 10ns; s <= '1';

end process;

END;
```

Final VHDL code

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

ENTITY datapath_tb IS

END datapath_tb;

ARCHITECTURE behavior OF datapath_tb IS

COMPONENT register_final

PORT(

    src_s1 : IN std_logic; src_s2 : IN std_logic; src_s3 : IN std_logic;

    des_a1 : IN std_logic; des_a2 : IN std_logic; des_a3 : IN std_logic;

    data_load : IN std_logic; clk : IN std_logic;

    data : IN std_logic_vector(15 downto 0);

    Q : OUT std_logic_vector(15 downto 0);

    r1 : OUT std_logic_vector(15 downto 0);

    r2 : OUT std_logic_vector(15 downto 0);

    r3 : OUT std_logic_vector(15 downto 0);

    r4 : OUT std_logic_vector(15 downto 0);

    r5 : OUT std_logic_vector(15 downto 0);

    r6 : OUT std_logic_vector(15 downto 0);

    r7 : OUT std_logic_vector(15 downto 0);

    r8 : OUT std_logic_vector(15 downto 0) );

END COMPONENT;

signal src_s1 : std_logic := '0';

signal src_s2 : std_logic := '0';

signal src_s3 : std_logic := '0';

signal des_a1 : std_logic := '0';

signal des_a2 : std_logic := '0';

signal des_a3 : std_logic := '0';

signal data_load : std_logic := '0';

signal clk : std_logic := '0';

signal data : std_logic_vector(15 downto 0) := (others => '0');
```

```

signal Q : std_logic_vector(15 downto 0);
signal r1 : std_logic_vector(15 downto 0);
signal r2 : std_logic_vector(15 downto 0);
signal r3 : std_logic_vector(15 downto 0);
signal r4 : std_logic_vector(15 downto 0);
signal r5 : std_logic_vector(15 downto 0);
signal r6 : std_logic_vector(15 downto 0);
signal r7 : std_logic_vector(15 downto 0);
signal r8 : std_logic_vector(15 downto 0);
BEGIN
uut: register_final PORT MAP (
    src_s1 => src_s1, src_s2 => src_s2, src_s3 => src_s3,
    des_a1 => des_a1, des_a2 => des_a2, des_a3 => des_a3,
    data_load => data_load, clk => clk, data => data,
    Q => Q, r1 => r1, r2 => r2, r3 => r3, r4 => r4, r5 => r5, r6 => r6, r7 => r7, r8 => r8);
clk_process :process
begin
    clk <= '0';wait for clk_period/2; clk <= '1';wait for clk_period/2;
end process;
stim_proc: process
begin
    wait for 10ns; des_a1 <= '0'; des_a2 <= '0'; des_a3 <= '0'; data <= x"FFFF";
    wait for 10ns; des_a1 <= '0'; des_a2 <= '0'; des_a3 <= '1'; data <= x"EEEE";
    wait for 10ns; des_a1 <= '0'; des_a2 <= '1'; des_a3 <= '0'; data <= x"DDDD";
    wait for 10ns; des_a1 <= '0'; des_a2 <= '1'; des_a3 <= '1'; data <= x"CCCC";
    wait for 10ns; des_a1 <= '1'; des_a2 <= '0'; des_a3 <= '0'; data <= x"BBBB";
    wait for 10ns; des_a1 <= '1'; des_a2 <= '0'; des_a3 <= '1'; data <= x"AAAA";
    wait for 10ns; des_a1 <= '1'; des_a2 <= '1'; des_a3 <= '0'; data <= x"9999";
    wait for 10ns; des_a1 <= '1';des_a2 <= '1';des_a3 <= '1';data <= x"8888";
end process;
END;

```