


CS2022 PROJECT 2- MICROCODED INSTRUCTION SET PROCESSOR

Aniket Agarwal 17317437


Contents:

1. Results Of Test Benches
2. VHDL Component Source Code
3. Component Test Benches
1. Results of Test Benches


1.1 PROCESSOR FINAL FILE

 


1.1 ARITHMETIC LOGICAL UNIT

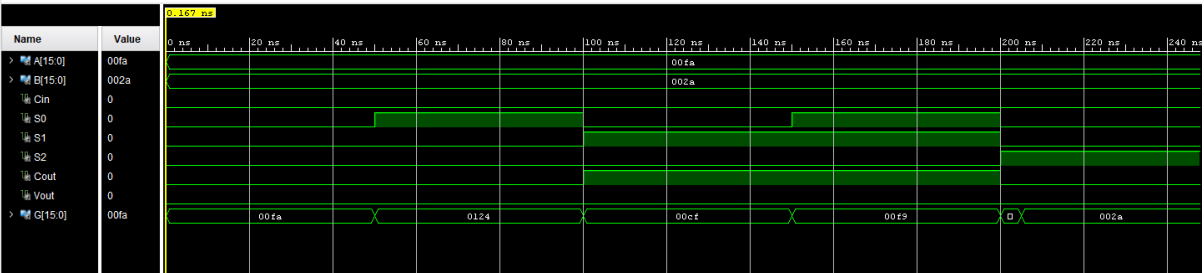


1.2 CONTROL ADDRESS REGISTER

 


1.3 EXTEND

 


1.4 INSTRUCTION REGISTER

 


1.5 MICROPROGRAMMED CONTROL

 


1.6 PROGRAM COUNTER

 


1.7 BARREL SHIFTER

 

1.8 CONTROL MEMORY

 


1.9 ARITHMETIC CIRCUIT

 


1.10 FUNCTIONAL UNIT




1.11 MEMORY

 


1.12 ZERO FILL

 


1.13 RIPPLE ADDER

 


1.14 REGISTER FILE

 


1.15 LOGIC CIRCUIT

 


1.16 DATAPATH

 


1.17 DECODER_3TO8

 


1.18 DECODER_4TO16

 


1.19 MUX16_16BIT

 


1.20 MUX16_1BIT

 


1.21 MUX2_1_16BIT

 


1.22 MUX2_1_8BIT

 


1.23 MUX8_16BIT

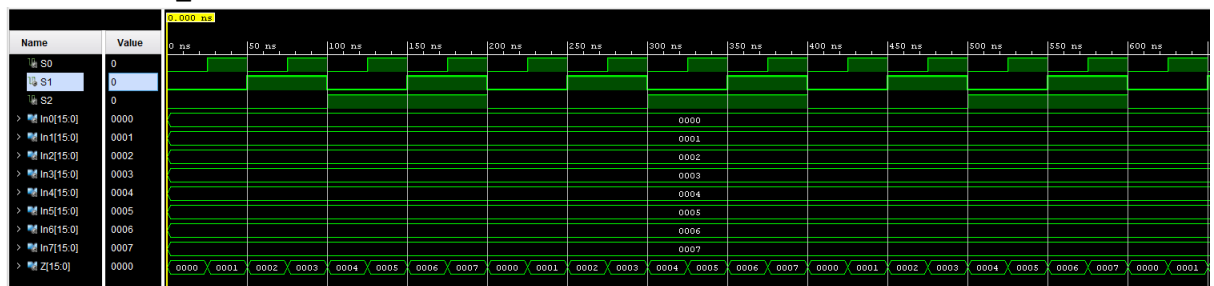


1.24 MUX8_1BIT

 


1.25 FULL ADDER

 

1.26 MUXB_Y_16BIT

 


1.27 REGISTER

 


SCHEMATICS

COMPLETE PROJECT

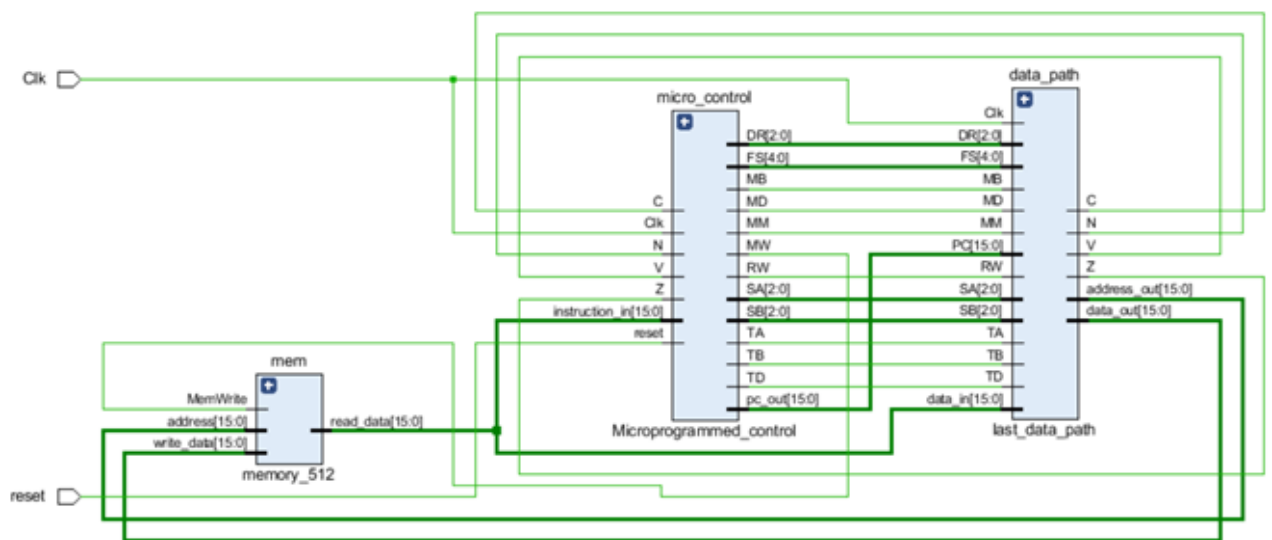

MICROPROGRAMMED CONTROLLER

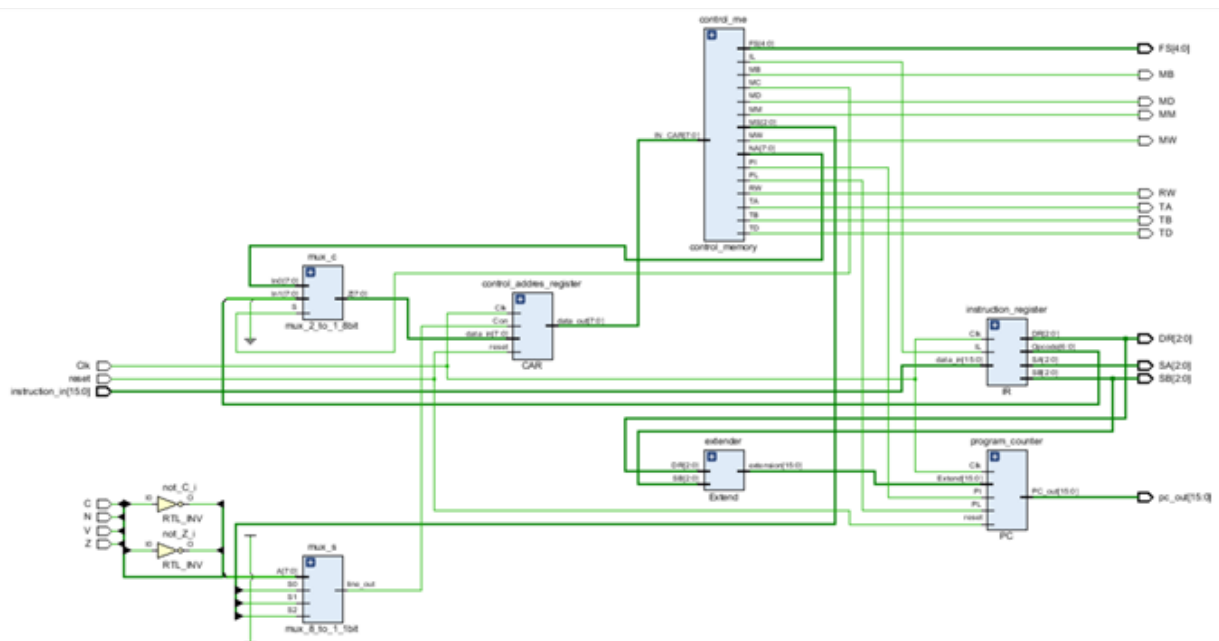



When turned on, the PC (program counter) and CAR (control address register) are both reset.

When the PC is reset it points to the first microprogram in memory. Memory contains the addresses of the instructions that are stored in control memory. For example, instruction 0x002E may correspond to the memory address in Control Memory of the instruction ADI. The address accessed is determined by the PC.

This microprogram (instruction) address is loaded into the IR (Instruction Register), where it is split into a 7-bit opcode (the first 7 bits) that corresponds to the instruction to be accessed in Control Memory, and three 3-bit values (the last 9 bits) that can either be used for register selection or as values (for immediate values or PC offset). They decide the Destination Register.

Opcode	DA	SA	SB
7 bit	3 bit	3 bit	3 bit

For example

ADD r0, r1, r2 =

0000011	000	001	010
= 00000110000001010 = 0x060A			

The opcode is loaded into MUX C, and, as the control memory is in the Instruction Fetch State, it is loaded from MUX C into the CAR and then used to select the next set of machine code in the Control Memory. The CAR determines what the next address the Control Memory uses to access the next instruction is.

The Control Memory accesses the instruction to be accessed (as dictated by CAR) based on the instruction address based in. An instruction could take more than one clock cycle (e.g Load).

The Control Memory controls the inputs to all of the multiplexers, Functional Unit, Register File, PC, IR, CAR and Memory.

Values coming from either the output of the Function unit or Memory (as selected by MUX D) can be loaded into registers in the Register File if RW (Read=0/Write=1) is set to high.

The Register File contains an array of registers which holds data. A temporary register (R8) is also here for multi-cycle instructions so that the data the user may be storing is not disrupted.

The destination register is selected by DR coming from IR, or TD (for the temp register) coming from Control Memory.

The Function Unit takes in values from the Register File (selected by SA, SB, TA or TB) or immediate values and performs arithmetic logic or shifting operations on those values. It contains an ALU & a Shifter. The status bits from the Function Unit are used for conditional instructions in the microprogrammed control.

Values from the Register File can also be stored in Memory M if MW(Memory Write) is set.

The processor is pipelined so that a number of operations can be happening simultaneously, i.e. instruction fetching, execution of a previous instruction and writing the results to the Register File.

2. VHDL Component Source Code

2.1 PROCESSOR FINAL

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity processor_final is
    Port(
        Clk : in STD_LOGIC;
        reset : in STD_LOGIC
    );
end processor_final;

architecture Behavioral of processor_final is

    COMPONENT Microprogrammed_control is
        Port ( instruction_in : in  STD_LOGIC_VECTOR (15 downto 0);
              reset : in STD_LOGIC;
              V : in  STD_LOGIC;
              C : in  STD_LOGIC;
              N : in  STD_LOGIC;
              Z : in  STD_LOGIC;
              Clk : in STD_LOGIC;
              pc_out : out STD_LOGIC_VECTOR (15 downto 0);
              DR : out  STD_LOGIC_VECTOR (2 downto 0);
              SA : out  STD_LOGIC_VECTOR (2 downto 0);
              SB : out  STD_LOGIC_VECTOR (2 downto 0);
              TD : out  STD_LOGIC;
              TA : out  STD_LOGIC;
              TB : out  STD_LOGIC;
              MB : out  STD_LOGIC;
              FS : out  STD_LOGIC_VECTOR (4 downto 0);
              MD : out  STD_LOGIC;
              RW : out  STD_LOGIC;
              MM : out  STD_LOGIC;
              MW : out  STD_LOGIC);
    end COMPONENT;

    COMPONENT last_data_path is
        Port ( PC : in  STD_LOGIC_VECTOR (15 downto 0);
              data_in : in  STD_LOGIC_VECTOR (15 downto 0);
              DR : IN  std_logic_vector(2 downto 0);
              SA : IN  std_logic_vector(2 downto 0);
              SB : IN  std_logic_vector(2 downto 0);
```

```

    TD : IN std_logic;
    TA : IN std_logic;
    TB : IN std_logic;
    Clk : in STD_LOGIC;
    FS : IN std_logic_vector(4 downto 0);
    RW : IN std_logic;
    MB : IN std_logic;
    MM : IN std_logic;
    MD : IN std_logic;
    data_out : out STD_LOGIC_VECTOR (15 downto 0);
    address_out : out STD_LOGIC_VECTOR (15 downto 0);
    V : out STD_LOGIC;
    C : out STD_LOGIC;
    N : out STD_LOGIC;
    Z : out STD_LOGIC);
end COMPONENT;

```

COMPONENT memory_512

```

    PORT(
        address : IN std_logic_vector(15 downto 0);
        write_data : IN std_logic_vector(15 downto 0);
        MemWrite : IN std_logic;
        read_data : OUT std_logic_vector(15 downto 0)
    );
END COMPONENT;

```

```

--signals
signal V_signal : std_logic;
signal C_signal : std_logic;
signal N_signal : std_logic;
signal Z_signal : std_logic;
signal TD_signal : std_logic;
signal TA_signal : std_logic;
signal TB_signal : std_logic;
signal MB_signal : std_logic;
signal MD_signal : std_logic;
signal RW_signal : std_logic;
signal MM_signal : std_logic;
signal MW_signal : std_logic;
signal DR_signal : std_logic_vector(2 downto 0);
signal SA_signal : std_logic_vector(2 downto 0);
signal SB_signal : std_logic_vector(2 downto 0);
signal FS_signal : std_logic_vector(4 downto 0);

```

```
signal datapath_address_out : std_logic_vector(15 downto 0);
signal datapath_data_out : std_logic_vector(15 downto 0);
signal memory_data_out : std_logic_vector(15 downto 0);
signal micro_pc_out : std_logic_vector(15 downto 0);
```

```
begin
```

```
micro_control : Microprogrammed_control PORT MAP (
    instruction_in => memory_data_out,
    reset => reset,
    V => V_signal,
    C => C_signal,
    N => N_signal,
    Z => Z_signal,
    Clk => Clk,
    pc_out => micro_pc_out,
    DR => DR_signal,
    SA => SA_signal,
    SB => SB_signal,
    TD => TD_signal,
    TA => TA_signal,
    TB => TB_signal,
    MB => MB_signal,
    FS => FS_signal,
    MD => MD_signal,
    RW => RW_signal,
    MM => MM_signal,
    MW => MW_signal
);
```

```
data_path : last_data_path PORT MAP (
    PC => micro_pc_out,
    data_in => memory_data_out,
    DR => DR_signal,
    SA => SA_signal,
    SB => SB_signal,
    TD => TD_signal,
    TA => TA_signal,
    TB => TB_signal,
    Clk => Clk,
    FS => FS_signal,
    RW => RW_signal,
    MB => MB_signal,
```

```

MM => MM_signal,
MD => MD_signal,
data_out => datapath_data_out,
address_out => datapath_address_out,
V => V_signal,
C => C_signal,
N => N_signal,
Z => Z_signal
);

```

```

mem : memory_512 PORT MAP (
    address => datapath_address_out,
    write_data => datapath_data_out,
    MemWrite => MW_signal,
    read_data => memory_data_out
);

```

```

end Behavioral;

```

2.2 ARITHMETIC LOGICAL UNIT

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ALU_unit_16bit is
    Port ( A : in  STD_LOGIC_VECTOR (15 downto 0);
          B : in  STD_LOGIC_VECTOR (15 downto 0);
          Cin : in  STD_LOGIC;
          S0 : in  STD_LOGIC;
          S1 : in  STD_LOGIC;
          S2 : in  STD_LOGIC;
          Cout : out STD_LOGIC;
          Vout : out STD_LOGIC;
          G : out  STD_LOGIC_VECTOR (15 downto 0));
end ALU_unit_16bit;

```

architecture Behavioral of ALU_unit_16bit is

```

COMPONENT arithmetic_circuit_16bit
PORT(
    Cin : IN  std_logic;
    S0 : IN  std_logic;

```

```

    S1 : IN std_logic;
    A : IN std_logic_vector(15 downto 0);
    B : IN std_logic_vector(15 downto 0);
    G : OUT std_logic_vector(15 downto 0);
    Cout : OUT std_logic;
    Vout : OUT std_logic
  );
END COMPONENT;

```

```

COMPONENT logic_circuit_16bit
PORT(
  A : IN std_logic_vector(15 downto 0);
  B : IN std_logic_vector(15 downto 0);
  s0 : IN std_logic;
  s1 : IN std_logic;
  Y : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;

```

```

COMPONENT mux_2_16bit
PORT(
  S : IN std_logic;
  In0 : IN std_logic_vector(15 downto 0);
  In1 : IN std_logic_vector(15 downto 0);
  Z : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;

```

```

-- signals
signal arith_out : std_logic_vector(15 downto 0);
signal logic_out : std_logic_vector(15 downto 0);

```

```
begin
```

```
--portmaps:
```

```
--arithmetic circuit
```

```
ac: arithmetic_circuit_16bit PORT MAP (
  Cin => Cin,
  S0 => S0,
  S1 => S1,
  A => A,
  B => B,

```

```

        G => arith_out,
        Cout => Cout,
        Vout => Vout
    );

--logical circuit
lc: logic_circuit_16bit PORT MAP (
    A => A,
    B => B,
    s0 => s0,
    s1 => s1,
    Y => logic_out
);

--2 to 1 multiplexer
mux: mux_2_16bit PORT MAP (
    S => s2,
    In0 => arith_out,
    In1 => logic_out,
    Z => G
);

```

end Behavioral;

2.3 CONTROL ADDRESS REGISTER

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity CAR is

Port (data_in : in STD_LOGIC_VECTOR (7 downto 0);

reset : in STD_LOGIC;

Con : in STD_LOGIC;

Clk : in STD_LOGIC;

data_out : out STD_LOGIC_VECTOR (7 downto 0));

end CAR;

architecture Behavioral of CAR is

```
COMPONENT ripple_adder_16bit
PORT(
    A : IN std_logic_vector(15 downto 0);
    B : IN std_logic_vector(15 downto 0);
    Cin : IN std_logic;
    S : OUT std_logic_vector(15 downto 0);
    Cout : OUT std_logic;
    Vout : OUT std_logic
);
END COMPONENT;
```

-- 16 bit Register

```
COMPONENT reg16
PORT(
    D : IN std_logic_vector(15 downto 0);
    load : IN std_logic;
    Clk : IN std_logic;
    Q : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;
```

```
signal increment : std_logic_vector(7 downto 0);
signal unused : std_logic_vector (7 downto 0);
signal current_val : std_logic_vector (15 downto 0);
signal into_reg : std_logic_vector (15 downto 0);
```

```
begin
```

```

-- ripple_adder_16bit
adder: ripple_adder_16bit PORT MAP(
    A(7 downto 0) => current_val(7 downto 0),
    A(15 downto 8) => x"00",
    B => x"0001",
    Cin => '0',
    S(7 downto 0) => increment,
    s(15 downto 8) => unused
);

-- register
reg: reg16 PORT MAP(
    D => into_reg,
    load => '1',
    Clk => Clk,
    Q => current_val
);

--into_reg(7 downto 0) <= x"C0" when reset='1' else data_in when Con = '1' else
increment;

into_reg(7 downto 0) <= data_in when Con = '1' else increment;
into_reg(15 downto 8) <= x"00";
data_out <= current_val(7 downto 0);

end Behavioral;

```


2.4 EXTEND

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity Extend is

Port (DR : in STD_LOGIC_VECTOR (2 downto 0);

SB : in STD_LOGIC_VECTOR (2 downto 0);

extension : out STD_LOGIC_VECTOR (15 downto 0));

end Extend;

architecture Behavioral of Extend is

begin

extension(15 downto 6) <= "0000000000" when (DR(2)='0') else "1111111111";

extension(5 downto 3) <= DR;

extension(2 downto 0) <= SB;

end Behavioral;

2.5 INSTRUCTION REGISTER

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity IR is

Port (data_in : in STD_LOGIC_VECTOR (15 downto 0);

IL : in STD_LOGIC;

Clk : in STD_LOGIC;

Opcode : out STD_LOGIC_VECTOR (6 downto 0);

DR : out STD_LOGIC_VECTOR (2 downto 0);

SA : out STD_LOGIC_VECTOR (2 downto 0);

```
        SB : out STD_LOGIC_VECTOR (2 downto 0));  
end IR;
```

architecture Behavioral of IR is

```
-- 16 bit Register  
COMPONENT reg16  
PORT(  
    D : IN std_logic_vector(15 downto 0);  
    load : IN std_logic;  
    Clk : IN std_logic;  
    Q : OUT std_logic_vector(15 downto 0)  
);  
END COMPONENT;
```

```
signal data_out : std_logic_vector(15 downto 0);
```

```
begin
```

```
-- register  
reg: reg16 PORT MAP(  
    D => data_in,  
    load => IL,  
    Clk => Clk,  
    Q => data_out  
);
```

```
Opcode<=data_out(15 downto 9);
```

```
DR<=data_out(8 downto 6);
```

```
SA<=data_out(5 downto 3);
```

```
SB<=data_out(2 downto 0);
```

```
end Behavioral;
```

2.6 MICROPROGRAMMED CONTROL

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity Microprogrammed_control is
```

```
Port ( instruction_in : in  STD_LOGIC_VECTOR (15 downto 0);
```

```
        reset : in STD_LOGIC;
```

```
        V : in  STD_LOGIC;
```

```
        C : in  STD_LOGIC;
```

```
        N : in  STD_LOGIC;
```

```
        Z : in  STD_LOGIC;
```

```
        Clk : in STD_LOGIC;
```

```
        pc_out : out  STD_LOGIC_VECTOR (15 downto 0);
```

```
        DR : out  STD_LOGIC_VECTOR (2 downto 0);
```

```
        SA : out  STD_LOGIC_VECTOR (2 downto 0);
```

```
        SB : out  STD_LOGIC_VECTOR (2 downto 0);
```

```
        TD : out  STD_LOGIC;
```

```
        TA : out  STD_LOGIC;
```

```
        TB : out  STD_LOGIC;
```

```
        MB : out  STD_LOGIC;
```

```
        FS : out  STD_LOGIC_VECTOR (4 downto 0);
```

```
        MD : out  STD_LOGIC;
```

```
        RW : out  STD_LOGIC;
```

```
        MM : out  STD_LOGIC;
```

```
        MW : out STD_LOGIC);  
end Microprogrammed_control;
```

architecture Behavioral of Microprogrammed_control is

COMPONENT PC

```
    PORT(  
        Extend : IN std_logic_vector(15 downto 0);  
        reset : IN std_logic;  
        PI : IN std_logic;  
        PL : IN std_logic;  
        Clk : IN std_logic;  
        PC_out : OUT std_logic_vector(15 downto 0)  
    );  
END COMPONENT;
```

COMPONENT mux_8_to_1_1bit

```
    PORT(  
        A : IN std_logic_vector(7 downto 0);  
        S0 : IN std_logic;  
        S1 : IN std_logic;  
        S2 : IN std_logic;  
        line_out : OUT std_logic  
    );  
END COMPONENT;
```

COMPONENT Extend

```

PORT(
    DR : IN std_logic_vector(2 downto 0);
    SB : IN std_logic_vector(2 downto 0);
    extension : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;

```

COMPONENT IR

```

PORT(
    data_in : IN std_logic_vector(15 downto 0);
    IL : IN std_logic;
    Clk : IN std_logic;
    Opcode : OUT std_logic_vector(6 downto 0);
    DR : OUT std_logic_vector(2 downto 0);
    SA : OUT std_logic_vector(2 downto 0);
    SB : OUT std_logic_vector(2 downto 0)
);
END COMPONENT;

```

COMPONENT mux_2_to_1_8bit

```

PORT(
    S : IN std_logic;
    In0 : IN std_logic_vector(7 downto 0);
    In1 : IN std_logic_vector(7 downto 0);
    Z : OUT std_logic_vector(7 downto 0)
);
END COMPONENT;

```

COMPONENT CAR

```
PORT(  
    data_in : IN std_logic_vector(7 downto 0);  
        reset : IN std_logic;  
        Clk : IN std_logic;  
    Con : IN std_logic;  
    data_out : OUT std_logic_vector(7 downto 0)  
);  
END COMPONENT;
```

COMPONENT control_memory

```
PORT(  
    MW : OUT std_logic;  
    MM : OUT std_logic;  
    RW : OUT std_logic;  
    MD : OUT std_logic;  
    FS : OUT std_logic_vector(4 downto 0);  
    MB : OUT std_logic;  
    TB : OUT std_logic;  
    TA : OUT std_logic;  
    TD : OUT std_logic;  
    PL : OUT std_logic;  
    PI : OUT std_logic;  
    IL : OUT std_logic;  
    MC : OUT std_logic;  
    MS : OUT std_logic_vector(2 downto 0);
```

```
    NA : OUT std_logic_vector(7 downto 0);  
    IN_CAR : IN std_logic_vector(7 downto 0)  
  );  
END COMPONENT;
```

```
    --signals
```

```
    signal MC : std_logic;  
    signal IL : std_logic;  
    signal PI : std_logic;  
    signal PL : std_logic;  
    signal not_Z : std_logic;  
    signal not_C : std_logic;  
    signal mux_s_out : std_logic;  
    signal MS : std_logic_vector(2 downto 0);  
    signal DR_signal : std_logic_vector(2 downto 0);  
    signal SA_signal : std_logic_vector(2 downto 0);  
    signal SB_signal : std_logic_vector(2 downto 0);  
    signal NA : std_logic_vector(7 downto 0);  
    signal mux_c_out : std_logic_vector(7 downto 0);  
    signal car_out : std_logic_vector(7 downto 0);  
    signal extend_out : std_logic_vector(15 downto 0);  
    signal ir_opcode_out : std_logic_vector(6 downto 0);
```

```
begin
```

```
extender : Extend PORT MAP (  
    DR => DR_signal,  
    SB => SB_signal,  
    extension => extend_out
```

);

program_counter : PC PORT MAP (

 Extend => extend_out,

 reset => reset,

 Clk => Clk,

 PL => PL,

 PI => PI,

 PC_out => pc_out

);

mux_s : mux_8_to_1_1bit PORT MAP (

 A(0) => '0',

 A(1) => '1',

 A(2) => C,

 A(3) => V,

 A(4) => Z,

 A(5) => N,

 A(6) => not_C,

 A(7) => not_Z,

 S0 => MS(0),

 S1 => MS(1),

 S2 => MS(2),

 line_out => mux_s_out

);

instruction_register : IR PORT MAP (

 data_in => instruction_in,


```

IL => IL,

        Clk => Clk,

Opcode => ir_opcode_out,

DR => DR_signal,

SA => SA_signal,

SB => SB_signal

);

```

```

mux_c : mux_2_to_1_8bit PORT MAP (

    In0 => NA,

        In1(7) => '0',

    In1(6 downto 0) => ir_opcode_out,

    S => MC,

    Z => mux_c_out

);

```

```

control_addres_register : CAR PORT MAP (

    data_in => mux_c_out,

        reset => reset,

        Clk => Clk,

    Con => mux_s_out,

    data_out => car_out

);

```

```

control_me : control_memory PORT MAP (

    MW => MW,

    MM => MM,

    RW => RW,

```

```

MD => MD,
FS => FS,
MB => MB,
TB => TB,
TA => TA,
TD => TD,
PL => PL,
PI => PI,
IL => IL,
MC => MC,
MS => MS,
NA => NA,
IN_CAR => car_out
);

```

```

DR <= DR_signal;
SB <= SB_signal;
SA <= SA_signal;
not_C <= not C;
not_Z <= not Z;
end Behavioral;

```

2.7 PROGRAM COUNTER

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity PC is
    Port ( Extend : in STD_LOGIC_VECTOR (15 downto 0);
          reset : in STD_LOGIC;

```

```

        Clk : in STD_LOGIC;

        PL : in STD_LOGIC;

        PI : in STD_LOGIC;

        PC_out : out STD_LOGIC_VECTOR (15 downto 0));
end PC;

```

architecture Behavioral of PC is

```

COMPONENT ripple_adder_16bit
PORT(
    A : IN std_logic_vector(15 downto 0);
    B : IN std_logic_vector(15 downto 0);
    Cin : IN std_logic;
    S : OUT std_logic_vector(15 downto 0);
    Cout : OUT std_logic;
    Vout : OUT std_logic
);
END COMPONENT;

```

-- 16 bit Register

```

COMPONENT reg16
PORT(
    D : IN std_logic_vector(15 downto 0);
    load : IN std_logic;
    Clk : IN std_logic;
    Q : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;

```

```
signal pi_or_pl_or_reset : std_logic;
signal load_result : std_logic_vector(15 downto 0);
signal increment_result : std_logic_vector(15 downto 0);
signal next_PC : std_logic_vector (15 downto 0);
signal last_PC : std_logic_vector (15 downto 0);
```

```
begin
```

```
-- ripple_adder_16bit
```

```
adderLoad: ripple_adder_16bit PORT MAP(
```

```
    A => last_pc,
```

```
    B(15 downto 0) => Extend,
```

```
    Cin => '0',
```

```
    S => load_result
```

```
);
```

```
-- ripple_adder_16bit
```

```
adderIncrement: ripple_adder_16bit PORT MAP(
```

```
    A => last_PC,
```

```
    B => x"0001",
```

```
    Cin => '0',
```

```
    S => increment_result
```

```
);
```

```
-- register
```

```
reg: reg16 PORT MAP(
```

```
    D => next_PC,
```

```
    load => pi_or_pl_or_reset,
```

```

    Clk => Clk,
    Q => last_PC
);

next_PC <= x"0000" when reset='1' else increment_result when PI='1' else
        load_result when PL='1' else x"0000";

PC_out <= last_PC;

pi_or_pl_or_reset <= (PI or PL or reset);

end Behavioral;

```

2.8 BARREL SHIFTER

--THIS BARRELL SHIFTER HAS BEEN ALTERED TO ONLY SHIFT ZERO BITS, 1 BIT LEFT OR 1 BIT RIGHT

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

entity barrel_shifter_16bit is
    Port ( B : in  STD_LOGIC_VECTOR (15 downto 0);
          S0 : in  STD_LOGIC;
          S1 : in  STD_LOGIC;
          S2 : in  STD_LOGIC;
          S3 : in  STD_LOGIC;
          F : out STD_LOGIC_VECTOR (15 downto 0));
end barrel_shifter_16bit;

```

```

architecture Behavioral of barrel_shifter_16bit is
    -- 16 to 1 line multiplexer
    COMPONENT mux16_1bit
    PORT(
        S0 : IN std_logic;
        S1 : IN std_logic;
        S2 : IN std_logic;
        S3 : IN std_logic;
        A : IN std_logic_vector(15 downto 0);
        F : OUT std_logic
    );

```

```

END COMPONENT;

signal fs_shift : std_logic_vector(3 downto 0);

begin
-- port maps ;-

-- mux 0
mux : for i in 0 to 15 generate

mux0to16: mux16_1bit PORT MAP(
    S0 => fs_shift(0),
    S1 => fs_shift(1),
    S2 => fs_shift(2),
    S3 => fs_shift(3),
    A(0) => B(i+0),
    A(1) => B((i+15) mod 16),
    A(2) => B((i+14) mod 16),
    A(3) => B((i+13) mod 16),
    A(4) => B((i+12) mod 16),
    A(5) => B((i+11) mod 16),
    A(6) => B((i+10) mod 16),
    A(7) => B((i+9) mod 16),
    A(8) => B((i+8) mod 16),
    A(9) => B((i+7) mod 16),
    A(10) => B((i+6) mod 16),
    A(11) => B((i+5) mod 16),
    A(12) => B((i+4) mod 16),
    A(13) => B((i+3) mod 16),
    A(14) => B((i+2) mod 16),
    A(15) => B((i+1) mod 16),
    F => F(i)
);
end generate;

fs_shift <= "0000" when (S0='0' and S1='0') else "1111" when (S0='0' and S1='1') else
"0001" when S0='1';

end Behavioral;

```

2.9 CONTROL MEMORY

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

```

```
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

entity control_memory is

```
Port (
    MW : out std_logic;
    MM : out std_logic;
    RW : out std_logic;
    MD : out std_logic;
    FS : out std_logic_vector(4 downto 0);
    MB : out std_logic;
    TB : out std_logic;
    TA : out std_logic;
    TD : out std_logic;
    PL : out std_logic;
    PI : out std_logic;
    IL : out std_logic;
    MC : out std_logic;
    MS : out std_logic_vector(2 downto 0);
    NA : out std_logic_vector(7 downto 0);
    IN_CAR : in std_logic_vector(7 downto 0));
end control_memory;
```

architecture Behavioral of control_memory is

```
type mem_array is array(0 to 255) of std_logic_vector(27 downto 0);
```

--Instruction	Address	Next Address	. MS	MC	IL	PI	PL
TD.TA TB	MB . FS	MD	RW	MM	MW	Code	

```

--      ADI      00      IF -> C0      001  0  0
0      0      0      0      0      1      00010 0      1      0      0      =
0xC020224

--      LD       01      IF -> C0      001  0
0      0      0      0      0      0      0      00000 1      1      0      0
=      0xC02000C

--      ST       02      IF -> C0      001  0
0      0      0      0      0      0      0      00000 0      0      0      1
=      0xC020001

--      INC      03      IF -> C0      001  0  0
0      0      0      0      0      0      00001 0      1      0      0      =
0xC020014

--      NOT      04      IF -> C0      001  0  0
0      0      0      0      0      0      01110 0      1      0      0      =
0xC0200E4

--      ADD      05      IF -> C0      001  0  0
0      0      0      0      0      0      00010 0      1      0      0      =
0xC020024

--      LRI      06      LRI2-> 86      001  0  0
0      0      0      0      0      0      00000 1      1      0      0      =
0x862000C

--      SR       07      SR2 -> 87      111  0
0      0      0      1      0      0      0      00000 0      1      0      0
=      0x87E1004

--      BEQ      09      B -> 30      100  0  0
0      1 1 1 1      0 10000      0      1      0      0      =      0x0081D04

--      Catch    0A      IF -> C0      001  0  0
0      0      0      0      0      0      00000 0      0      0      0      =
0xC020000

--      BNZ      0B      B -> 30      111  0  0
0      0      0      0      0      0      00000 0      0      0      0      =
0x30E0000

```



```

--      Catch      0C      IF -> C0      001  0  0
  0      0      0      0      0      0      00000 0      0      0      0      =
0xC020000

--      CMP      0D      IF -> C0      001  0  0
  0      0      1      0      0      0      00101 0      1      0      0      =
0xC021054

--      LR      29      IF -> C0      001  0  0
  0      0      0      0      0      0      00000 1      1      0      0      =
0xC02000C

--      B      30      IF -> C0      001  0
  0      0      1      0      0      0      0      00000 0      0      0      0
=      0xC022000

--      LRI2      86      IF -> C0      001  0  0
  0      0      0      1      0      0      00000 1      1      0      0      =
0xC02080C

--      SR2      87      SR3 -> 89      001  0  0
  0      0      0      0      0      0      10100 0      1      0      0      =
0x8820144

--      SR3      88      SR2 -> 87      100  0  0
  0      0      1      1      0      0      00110 0      1      0      0      =
0x8781864

--      Catch      89      IF -> C0      001  0  0
  0      0      0      0      0      0      00000 0      0      0      0      =
0xC020000

--      IF      C0      EXO -> C1      000  0
  1      1      0      0      0      0      0      00000 0      0      1      0
=      0xC10C002

--      EXO      C1      -- -> 00      001  1
  0      0      0      0      0      0      0      00000 0      0      0      0
=      0x0030000

```

begin

memory_m: process(IN_CAR)

variable control_mem : mem_array:=

X"C020224", -- 0x00	ADI: Add immediate constant
X"C02000C", -- 0x01	LD: Load
X"C020001", -- 0x02	ST: Store
X"C020014", -- 0x03	INC: Increment
X"C0200E4", -- 0x04	NOT: Not
X"C020024", -- 0x05	ADD: Add
X"862000C", -- 0x06	LRI: Load into immediate register Micro operation 1
X"87E1004", -- 0x07	SR: Shift Right
Micro-operation 1	
X"C020000", -- 0x08	Catch (to fall through to if shifted right by zero)
X"3080000", -- 0x09	BEQ: Branch if equal
X"C020000", -- 0x0A	Catch (to fall through to if branch not taken)
X"30E0000", -- 0x0B	BNZ: Branch if not zero
X"C020000", -- 0x0C	Catch (to fall through to if branch not taken)
X"C021054", -- 0x0D	CMP: Compare
X"0000000", -- 0x0E	
X"0000000", -- 0x0F	
X"0000000", -- 0x10	
X"0000000", -- 0x11	
X"0000000", -- 0x12	
X"0000000", -- 0x13	
X"0000000", -- 0x14	
X"0000000", -- 0x15	
X"0000000", -- 0x16	

X"0000000", -- 0x17

X"0000000", -- 0x18

X"0000000", -- 0x19

X"0000000", -- 0x1A

X"0000000", -- 0x1B

X"0000000", -- 0x1C

X"0000000", -- 0x1D

X"0000000", -- 0x1E

X"0000000", -- 0x1F

X"0000000", -- 0x20

X"0000000", -- 0x21

X"0000000", -- 0x22

X"0000000", -- 0x23

X"0000000", -- 0x24

X"0000000", -- 0x25

X"0000000", -- 0x26

X"0000000", -- 0x27

X"0000000", -- 0x28

X"C02000C", -- 0x29 LR: Load

X"0000000", -- 0x2A

X"0000000", -- 0x2B

X"0000000", -- 0x2C

X"0000000", -- 0x2D

X"0000000", -- 0x2E

X"0000000", -- 0x2F

X"C022000", -- 0x30 B: Unconditional Branch

X"0000000", -- 0x31

X"0000000", -- 0x32

X"0000000", -- 0x33

X"0000000", -- 0x34

X"0000000", -- 0x35

X"0000000", -- 0x36

X"0000000", -- 0x37

X"0000000", -- 0x38

X"0000000", -- 0x39

X"0000000", -- 0x3A

X"0000000", -- 0x3B

X"0000000", -- 0x3C

X"0000000", -- 0x3D

X"0000000", -- 0x3E

X"0000000", -- 0x3F

X"0000000", -- 0x40

X"0000000", -- 0x41

X"0000000", -- 0x42

X"0000000", -- 0x43

X"0000000", -- 0x44

X"0000000", -- 0x45

X"0000000", -- 0x46

X"0000000", -- 0x47

X"0000000", -- 0x48

X"0000000", -- 0x49

X"0000000", -- 0x4A

X"0000000", -- 0x4B

X"0000000", -- 0x4C

X"0000000", -- 0x4D

X"0000000", -- 0x4E

X"0000000", -- 0x4F

X"0000000", -- 0x50

X"0000000", -- 0x51

X"0000000", -- 0x52

X"0000000", -- 0x53

X"0000000", -- 0x54

X"0000000", -- 0x55

X"0000000", -- 0x56

X"0000000", -- 0x57

X"0000000", -- 0x58

X"0000000", -- 0x59

X"0000000", -- 0x5A

X"0000000", -- 0x5B

X"0000000", -- 0x5C

X"0000000", -- 0x5D

X"0000000", -- 0x5E

X"0000000", -- 0x5F

X"0000000", -- 0x60

X"0000000", -- 0x61

X"0000000", -- 0x62

X"0000000", -- 0x63

X"0000000", -- 0x64

X"0000000", -- 0x65

X"0000000", -- 0x66

X"0000000", -- 0x67

X"0000000", -- 0x68

X"0000000", -- 0x69

X"0000000", -- 0x6A

X"0000000", -- 0x6B

X"0000000", -- 0x6C

X"0000000", -- 0x6D

X"0000000", -- 0x6E

X"0000000", -- 0x6F

X"0000000", -- 0x70

X"0000000", -- 0x71

X"0000000", -- 0x72

X"0000000", -- 0x73

X"0000000", -- 0x74

X"0000000", -- 0x75

X"0000000", -- 0x76

X"0000000", -- 0x77

X"0000000", -- 0x78

X"0000000", -- 0x79

X"0000000", -- 0x7A

X"0000000", -- 0x7B

X"0000000", -- 0x7C

X"0000000", -- 0x7D

X"0000000", -- 0x7E

X"0000000", -- 0x7F

X"0000000", -- 0x80

X"0000000", -- 0x81

X"0000000", -- 0x82

X"0000000", -- 0x83

X"0000000", -- 0x84

X"0000000", -- 0x85

X"C02080C", -- 0x86

LRI2: Load Immediate Register Micro-operation 2

X"8820144", -- 0x87

SRM2: Shift Register Micro-operation 2

X"8781864", -- 0x88

SRM3: Shift Register Micro-operation 3

X"C020000", -- 0x89

Catch (to fall through to if finished shifting right)

X"0000000", -- 0x8A

X"0000000", -- 0x8B

X"0000000", -- 0x8C

X"0000000", -- 0x8D

X"0000000", -- 0x8E

X"0000000", -- 0x8F

X"0000000", -- 0x90

X"0000000", -- 0x91

X"0000000", -- 0x92

X"0000000", -- 0x93

X"0000000", -- 0x94

X"0000000", -- 0x95

X"0000000", -- 0x96

X"0000000", -- 0x97

X"0000000", -- 0x98

X"0000000", -- 0x99

X"0000000", -- 0x9A

X"0000000", -- 0x9B

X"0000000", -- 0x9C

X"0000000", -- 0x9D

X"0000000", -- 0x9E

X"0000000", -- 0x9F

X"0000000", -- 0xA0
X"0000000", -- 0xA1
X"0000000", -- 0xA2
X"0000000", -- 0xA3
X"0000000", -- 0xA4
X"0000000", -- 0xA5
X"0000000", -- 0xA6
X"0000000", -- 0xA7
X"0000000", -- 0xA8
X"0000000", -- 0xA9
X"0000000", -- 0xAA
X"0000000", -- 0xAB
X"0000000", -- 0xAC
X"0000000", -- 0xAD
X"0000000", -- 0xAE
X"0000000", -- 0xAF

X"0000000", -- 0xB0
X"0000000", -- 0xB1
X"0000000", -- 0xB2
X"0000000", -- 0xB3
X"0000000", -- 0xB4
X"0000000", -- 0xB5
X"0000000", -- 0xB6
X"0000000", -- 0xB7
X"0000000", -- 0xB8
X"0000000", -- 0xB9
X"0000000", -- 0xBA

X"0000000", -- 0xBB

X"0000000", -- 0xBC

X"0000000", -- 0xBD

X"0000000", -- 0xBE

X"0000000", -- 0xBF

X"C10C002", -- 0xC0 Instruction fetch

X"0030000", -- 0xC1 EXO

X"0000000", -- 0xC2

X"0000000", -- 0xC3

X"0000000", -- 0xC4

X"0000000", -- 0xC5

X"0000000", -- 0xC6

X"0000000", -- 0xC7

X"0000000", -- 0xC8

X"0000000", -- 0xC9

X"0000000", -- 0xCA

X"0000000", -- 0xCB

X"0000000", -- 0xCC

X"0000000", -- 0xCD

X"0000000", -- 0xCE

X"0000000", -- 0xCF

X"0000000", -- 0xD0

X"0000000", -- 0xD1

X"0000000", -- 0xD2

X"0000000", -- 0xD3

X"0000000", -- 0xD4

X"0000000", -- 0xD5

X"0000000", -- 0xD6

X"0000000", -- 0xD7

X"0000000", -- 0xD8

X"0000000", -- 0xD9

X"0000000", -- 0xDA

X"0000000", -- 0xDB

X"0000000", -- 0xDC

X"0000000", -- 0xDD

X"0000000", -- 0xDE

X"0000000", -- 0xDF

X"0000000", -- 0xE0

X"0000000", -- 0xE1

X"0000000", -- 0xE2

X"0000000", -- 0xE3

X"0000000", -- 0xE4

X"0000000", -- 0xE5

X"0000000", -- 0xE6

X"0000000", -- 0xE7

X"0000000", -- 0xE8

X"0000000", -- 0xE9

X"0000000", -- 0xEA

X"0000000", -- 0xEB

X"0000000", -- 0xEC

X"0000000", -- 0xED

X"0000000", -- 0xEE

X"0000000", -- 0xEF

X"0000000", -- 0xF0

X"0000000", -- 0xF1

X"0000000", -- 0xF2

X"0000000", -- 0xF3

X"0000000", -- 0xF4

X"0000000", -- 0xF5

X"0000000", -- 0xF6

X"0000000", -- 0xF7

X"0000000", -- 0xF8

X"0000000", -- 0xF9

X"0000000", -- 0xFA

X"0000000", -- 0xFB

X"0000000", -- 0xFC

X"0000000", -- 0xFD

X"0000000", -- 0xFE

X"0000000" -- 0xFF

);

variable addr : integer;

variable control_out : std_logic_vector(27 downto 0);

begin

addr := conv_integer(IN_CAR);

control_out := control_mem(addr);

MW <= control_out(0);

MM <= control_out(1);

RW <= control_out(2);

MD <= control_out(3);

FS <= control_out(8 downto 4);

MB <= control_out(9);

TB <= control_out(10);

```

    TA <= control_out(11);

    TD <= control_out(12);

    PL <= control_out(13);

    PI <= control_out(14);

    IL <= control_out(15);

    MC <= control_out(16);

    MS <= control_out(19 downto 17);

    NA <= control_out(27 downto 20);

    end process;

end Behavioral;

```

2.10 ARITHMETIC CIRCUIT

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

entity arithmetic_circuit_16bit is

```

```

    Port ( Cin : in  STD_LOGIC;
          S0 : in  STD_LOGIC;
          S1 : in  STD_LOGIC;
          A : in  STD_LOGIC_VECTOR (15 downto 0);
          B : in  STD_LOGIC_VECTOR (15 downto 0);
          G : out STD_LOGIC_VECTOR (15 downto 0);
          Cout : out STD_LOGIC;
          Vout : out STD_LOGIC);

```

```

end arithmetic_circuit_16bit;

```

```

architecture Behavioral of arithmetic_circuit_16bit is

```

```

-- components

```

```

    COMPONENT ripple_adder_16bit

```

```

    PORT(

```

```

        A : IN std_logic_vector(15 downto 0);
        B : IN std_logic_vector(15 downto 0);
        Cin : IN std_logic;
        S : OUT std_logic_vector(15 downto 0);
        Cout : OUT std_logic;
        Vout : OUT std_logic
    );

```

```
END COMPONENT;
```

```
COMPONENT b_to_y_16bit
PORT(
    B : IN std_logic_vector(15 downto 0);
    S0 : IN std_logic;
    S1 : IN std_logic;
    Y : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;
```

```
--signals
signal from_logic_to_adder : std_logic_vector(15 downto 0);
```

```
begin
-- port maps ;-)
```

```
-- ripple_adder_16bit
adder: ripple_adder_16bit PORT MAP(
    A => A,
    B => from_logic_to_adder,
    Cin => Cin,
    S => G,
    Cout => Cout,
    Vout => Vout
);
```

```
-- b_to_y_16bit
bitslice_logic: b_to_y_16bit PORT MAP(
    B => B,
    S0 => S0,
    S1 => S1,
    Y => from_logic_to_adder
);
```

```
end Behavioral;
```

2.11 FUNCTIONAL UNIT

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

entity functional_unit_16bit is

Port (FSS : in STD_LOGIC_VECTOR (4 downto 0);

A : in STD_LOGIC_VECTOR (15 downto 0);

B : in STD_LOGIC_VECTOR (15 downto 0);

F : out STD_LOGIC_VECTOR (15 downto 0);

V : out STD_LOGIC;

C : out STD_LOGIC;

N : out STD_LOGIC;

Z : out STD_LOGIC);

end functional_unit_16bit;

architecture Behavioral of functional_unit_16bit is

COMPONENT ALU_unit_16bit

PORT(

A : IN std_logic_vector(15 downto 0);

B : IN std_logic_vector(15 downto 0);

Cin : IN std_logic;

S0 : IN std_logic;

S1 : IN std_logic;

S2 : IN std_logic;

Cout : OUT std_logic;

Vout : OUT std_logic;

G : OUT std_logic_vector(15 downto 0)

);

END COMPONENT;

COMPONENT barrel_shifter_16bit

```

PORT(
    B : IN std_logic_vector(15 downto 0);
    S0 : IN std_logic;
    S1 : IN std_logic;
    S2 : IN std_logic;
    S3 : IN std_logic;
    F : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;

```

```

COMPONENT mux_2_16bit
PORT(
    S : IN std_logic;
    In0 : IN std_logic_vector(15 downto 0);
    In1 : IN std_logic_vector(15 downto 0);
    Z : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;

```

--Inputs

```

signal S0 : std_logic := '0';
signal S1 : std_logic := '0';
signal S2 : std_logic := '0';
signal S3 : std_logic := '0';

signal In0 : std_logic_vector(15 downto 0) := (others => '0');
signal In1 : std_logic_vector(15 downto 0) := (others => '0');

```

--Outputs

signal Cout : std_logic;

signal Vout : std_logic;

signal alu_out : std_logic_vector(15 downto 0);

signal shift_out : std_logic_vector(15 downto 0);

begin

--ALU

aluu: ALU_unit_16bit PORT MAP (

A => A,

B => B,

Cin => FSS(0),--carry only used for some operations determined by FS

S0 => FSS(1),

S1 => FSS(2),

S2 => FSS(3),

Cout => C,

Vout => V,

G => alu_out

);

--shifter

shifter: barrel_shifter_16bit PORT MAP (

B => B,

S0 => FSS(3),

S1 => FSS(2),

S2 => FSS(1),

S3 => FSS(0),

F => shift_out

);

--mux


```

mux: mux_2_16bit PORT MAP (
    S => FSS(4),
    In0 => alu_out,
    In1 => shift_out,
    Z => F
);

```

```

Z <= '1' when (alu_out=x"0000") else '0';
N <= alu_out(15);
end Behavioral;

```

2.12 MEMORY

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.ALL;

```

entity memory_512 is

```

    Port ( address : in  STD_LOGIC_VECTOR (15 downto 0);
          write_data : in  STD_LOGIC_VECTOR (15 downto 0);
          --Clk : in STD_LOGIC;

          MemWrite : in  STD_LOGIC;
          read_data : out STD_LOGIC_VECTOR (15 downto 0));

```

end memory_512;

architecture Behavioral of memory_512 is

```

type mem_array is array(0 to 511) of std_logic_vector(15 downto 0);
-- define type, for memory arrays
signal snl : unsigned(15 downto 0);

```

```

signal clk11 : std_logic;

begin

snl <= unsigned(address);

mem_process: process (address, write_data)

-- initialize data memory, X denotes hexadecimal number

variable data_mem : mem_array := (

```

	PC	Instructions
	Pseudocode	
Codewords		Hex
		Opcode DR SA SB
X"00DB", --0000		ADI R3, R3, #3
R3 = (0 + 3) = 3		0000000 011 011 011
00DB		
X"0ADB", --0001		ADD R3, R3, R3
R3 = (3 + 3) = 6		0000101 011 011
011	0ADB	
X"0121", --0010		ADI R4, R4, #1
R4 = (0 + 1) = 1		0000000 100 100 001
0121		
X"0F24", --0011		SR R4, R4, R4
R4 = (1 >> 1) = 0x8000		0000111 100 100 100
0F24		
X"0ADB", --0100		ADD R3, R3, R3
R3 = (6 + 6) = 12		0000101 011 011 011
0ADB		
X"03D8", --0101		LD R7, Memory[R3]
= Memory[12] = 0x00FF		0000001 111 011 000
		03D8
X"08D8", --0110		NOT R3, R3
R3 = (~12) = 0xFFFF3		0000100 011 011 000
08D8		

X"06D8", --0111	while	INC R3, R3	
4x(R3 = R3 + 1) = 0			0000011 011 011 000
06D8			

X"17C6", --1000		BNZ while
-----------------	--	-----------

0001011 111 000 110	17C6
---------------------	------

X"3A00", --1001	stop	B stop
-----------------	------	--------

0011101 000 000 000	3A00
---------------------	------

X"0000", --	State now
= [R3==0 R4==0x8000 R7==0xFF]	

X"0000", --

X"00FF", --(Memory[12])

X"0000", --

X"0000", --

X"0000", --

X"0000", X"0000", X"0000",X"0000",	--x0010 - x001F
------------------------------------	-----------------

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",	--x0020 - x002F
------------------------------------	-----------------

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",	--x0030 - x003F
------------------------------------	-----------------

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000",X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000",X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",

--x0040 - x004F

X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000",X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",

--x0050 - x005F

X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000",X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",

--x0060 - x006F

X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000",X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",

--x0070 - x007F

X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000",X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",

--x0080 - x008F

X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000",X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",

--x0090 - x009F

X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000",X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",

--x00A0 - x00AF

X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000",X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",

--x00A0 - x00AF

X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000",X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",

--x00B0 - x00BF

X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000",X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",

--x00C0 - x00CF

X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000",X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",

--x00D0 - x00DF

X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000",X"0000",X"0000",

--x00F0 - x00FF

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",

--x0100 - x010F

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000",X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",

--x0110 - x011F

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000",X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",

--x0120 - x012F

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000",X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",

--x0130 - x013F

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000",X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",

--x0140 - x014F

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000",X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",

--x0150 - x015F

X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000",X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",

X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000",X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",

--x0160 - x016F

X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000",X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",

--x0170 - x017F

X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000",X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",

--x0180 - x018F

X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000",X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",

--x0190 - x019F

X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",
X"0000", X"0000",X"0000",X"0000",
X"0000", X"0000", X"0000",X"0000",

--x01A0 - x01AF

X"0000", X"0000", X"0000",X"0000",

--x01A0 - x01AF

```
X"0000", X"0000", X"0000",X"0000",  
X"0000", X"0000",X"0000",X"0000",  
X"0000", X"0000", X"0000",X"0000",
```

```
X"0000", X"0000", X"0000",X"0000",      --x01B0 - x01BF  
X"0000", X"0000", X"0000",X"0000",  
X"0000", X"0000",X"0000",X"0000",  
X"0000", X"0000", X"0000",X"0000",
```

```
X"0000", X"0000", X"0000",X"0000",      --x01C0 - x01CF  
X"0000", X"0000", X"0000",X"0000",  
X"0000", X"0000",X"0000",X"0000",  
X"0000", X"0000", X"0000",X"0000",
```

```
X"0000", X"0000", X"0000",X"0000",      --x01D0 - x01DF  
X"0000", X"0000", X"0000",X"0000",  
X"0000", X"0000",X"0000",X"0000",  
X"0000", X"0000", X"0000",X"0000",
```

```
X"0000", X"0000", X"0000",X"0000",      --x01F0 - x01FF  
X"0000", X"0000", X"0000",X"0000",  
X"0000", X"0000",X"0000",X"0000",  
X"0000", X"0000", X"0000",X"0000" );
```

```
variable addr:integer;
```

```
begin -- the following type conversion function is in std_logic_arith
```

```
snl <= unsigned(address);
```

```
addr:= to_integer(snl(6 downto 0));
```



```

if MemWrite ='1' then
data_mem(addr):= write_data;
end if;
read_data<=data_mem(addr);

end process;

end Behavioral;

```

2.13 ZERO-FILL

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity zero_fill is
    Port ( SB : in  STD_LOGIC_VECTOR (2 downto 0);
          constant_out : out STD_LOGIC_VECTOR (15 downto 0));
end zero_fill;

```

architecture Behavioral of zero_fill is

```

begin
constant_out(2 downto 0) <= SB;
constant_out(15 downto 3) <= "00000000000000";
end Behavioral;

```

2.14 RIPPLE ADDER

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

entity ripple_adder_16bit is

Port (A : in STD_LOGIC_VECTOR (15 downto 0);

B : in STD_LOGIC_VECTOR (15 downto 0);

Cin : in STD_LOGIC;

Cout : out STD_LOGIC;

Vout : out STD_LOGIC;

S : out STD_LOGIC_VECTOR (15 downto 0));

end ripple_adder_16bit;

architecture Behavioral of ripple_adder_16bit is

-- components

COMPONENT full_adder

PORT(

A : IN std_logic;

B : IN std_logic;

Cin : IN std_logic;

S : OUT std_logic;

Cout : OUT std_logic

);

END COMPONENT;

-- signals

-- each c(i) is the carry going into adder(i) except c(0) which is the final carry

signal c : std_logic_vector(15 downto 0);

begin

-- port maps ;-)

-- adder 0

add00: full_adder PORT MAP(

 A => A(0),

 B => B(0),

 Cin => Cin,

 S => S(0),

 Cout => c(1)

);

-- adder 1

add01: full_adder PORT MAP(

 A => A(1),

 B => B(1),

 Cin => c(1),

 S => S(1),

 Cout => c(2)

);

-- adder 2

add02: full_adder PORT MAP(

 A => A(2),

 B => B(2),

 Cin => c(2),

 S => S(2),

 Cout => c(3)

);

-- adder 3

add03: full_adder PORT MAP(

 A => A(3),

 B => B(3),

 Cin => c(3),

```

        S => S(3),

        Cout => c(4)

    );

-- adder 4
add04: full_adder PORT MAP(

    A => A(4),

    B => B(4),

    Cin => c(4),

    S => S(4),

    Cout => c(5)

);

-- adder 5
add05: full_adder PORT MAP(

    A => A(5),

    B => B(5),

    Cin => c(5),

    S => S(5),

    Cout => c(6)

);

-- adder 6
add06: full_adder PORT MAP(

    A => A(6),

    B => B(6),

    Cin => c(6),

    S => S(6),

    Cout => c(7)

);

-- adder 7
add07: full_adder PORT MAP(

```

```

    A => A(7),
    B => B(7),
    Cin => c(7),
    S => S(7),
    Cout => c(8)
);

-- adder 8
add08: full_adder PORT MAP(
    A => A(8),
    B => B(8),
    Cin => c(8),
    S => S(8),
    Cout => c(9)
);

-- adder 9
add09: full_adder PORT MAP(
    A => A(9),
    B => B(9),
    Cin => c(9),
    S => S(9),
    Cout => c(10)
);

-- adder 10
add10: full_adder PORT MAP(
    A => A(10),
    B => B(10),
    Cin => c(10),
    S => S(10),
    Cout => c(11)
);

```

```
);  
  
-- adder 11  
add11: full_adder PORT MAP(  
    A => A(11),  
    B => B(11),  
    Cin => c(11),  
    S => S(11),  
    Cout => c(12)  
);  
  
-- adder 12  
add12: full_adder PORT MAP(  
    A => A(12),  
    B => B(12),  
    Cin => c(12),  
    S => S(12),  
    Cout => c(13)  
);  
  
-- adder 13  
add13: full_adder PORT MAP(  
    A => A(13),  
    B => B(13),  
    Cin => c(13),  
    S => S(13),  
    Cout => c(14)  
);  
  
-- adder 14  
add14: full_adder PORT MAP(  
    A => A(14),  
    B => B(14),
```

```

        Cin => c(14),
        S => S(14),
        Cout => c(15)
    );
-- adder 15
add15: full_adder PORT MAP(
    A => A(15),
    B => B(15),
    Cin => c(15),
    S => S(15),
    Cout => c(0)
);
Vout <= (c(15) xor c(0));
Cout <= c(0);
end Behavioral;

```

2.15 REGISTER FILE

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity new_reg_file_9x16bit is
    Port ( des_sel : in STD_LOGIC_VECTOR (2 downto 0);
          a_sel : in STD_LOGIC_VECTOR (2 downto 0);
          b_sel : in STD_LOGIC_VECTOR (2 downto 0);
          TD : in STD_LOGIC;
          TA : in STD_LOGIC;
          TB : in STD_LOGIC;
          load_enable : in STD_LOGIC;
          reset : in std_logic;

```

```

    Clk : in STD_LOGIC;

    input_data : in STD_LOGIC_VECTOR (15 downto 0);

    a_data : out STD_LOGIC_VECTOR (15 downto 0);

    b_data : out STD_LOGIC_VECTOR (15 downto 0));

end new_reg_file_9x16bit;

```

architecture Behavioral of new_reg_file_9x16bit is

-- components

-- 16 bit Register for register file

COMPONENT reg16

PORT(

 D : IN std_logic_vector(15 downto 0);

 load : IN std_logic;

 Clk : IN std_logic;

 Q : OUT std_logic_vector(15 downto 0)

);

END COMPONENT;

-- 3 to 8 Decoder

COMPONENT decoder_4to16

PORT(

 A0 : IN std_logic;

 A1 : IN std_logic;

 A2 : IN std_logic;

 A3 : IN std_logic;

 Q0 : OUT std_logic;

 Q1 : OUT std_logic;

 Q2 : OUT std_logic;

 Q3 : OUT std_logic;


```

        Q4 : OUT std_logic;
        Q5 : OUT std_logic;
        Q6 : OUT std_logic;
        Q7 : OUT std_logic;
        Q8 : OUT std_logic;
        Q9 : OUT std_logic;
        Q10 : OUT std_logic;
        Q11 : OUT std_logic;
        Q12 : OUT std_logic;
        Q13 : OUT std_logic;
        Q14 : OUT std_logic;
        Q15 : OUT std_logic
    );
END COMPONENT;

```

-- 2 to 1 line multiplexer

```

COMPONENT mux_2_16bit
PORT(
    In0 : IN std_logic_vector(15 downto 0);
    In1 : IN std_logic_vector(15 downto 0);
    s : IN std_logic;
    Z : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;

```

-- 16 to 1 line multiplexer

```

COMPONENT mux16_16bit
PORT(
    In0 : IN std_logic_vector(15 downto 0);

```

```

    In1 : IN std_logic_vector(15 downto 0);
    In2 : IN std_logic_vector(15 downto 0);
    In3 : IN std_logic_vector(15 downto 0);
    In4 : IN std_logic_vector(15 downto 0);
    In5 : IN std_logic_vector(15 downto 0);
    In6 : IN std_logic_vector(15 downto 0);
    In7 : IN std_logic_vector(15 downto 0);
    In8 : IN std_logic_vector(15 downto 0);
    In9 : IN std_logic_vector(15 downto 0);
    In10 : IN std_logic_vector(15 downto 0);
    In11 : IN std_logic_vector(15 downto 0);
    In12 : IN std_logic_vector(15 downto 0);
    In13 : IN std_logic_vector(15 downto 0);
    In14 : IN std_logic_vector(15 downto 0);
    In15 : IN std_logic_vector(15 downto 0);

    S0 : IN std_logic;
    S1 : IN std_logic;
    S2 : IN std_logic;
    S3 : IN std_logic;

    Z : OUT std_logic_vector(15 downto 0)
    );

END COMPONENT;

-- signals
signal d_data : std_logic_vector(15 downto 0);
signal load_reg0, load_reg1, load_reg2, load_reg3,
load_reg4, load_reg5, load_reg6, load_reg7, load_reg8, load_reg9, load_reg10,
load_reg11, load_reg12, load_reg13, load_reg14, load_reg15 : std_logic;
signal reg0_q, reg1_q, reg2_q, reg3_q,

```

```

    reg4_q, reg5_q, reg6_q, reg7_q, reg8_q, reg9_q, reg10_q,
    reg11_q, reg12_q, reg13_q, reg14_q, reg15_q : std_logic_vector(15 downto 0);
    signal write_reg0, write_reg1, write_reg2, write_reg3,
    write_reg4, write_reg5, write_reg6, write_reg7, write_reg8, write_reg9,
    write_reg10,
    write_reg11, write_reg12, write_reg13, write_reg14, write_reg15 : std_logic;

begin

-- port maps ;-)

-- register 0
reg00: reg16 PORT MAP(
    D => d_data,
    load => write_reg0,
    Clk => Clk,
    Q => reg0_q
);

-- register 1
reg01: reg16 PORT MAP(
    D => d_data,
    load => write_reg1,
    Clk => Clk,
    Q => reg1_q
);

-- register 2
reg02: reg16 PORT MAP(
    D => d_data,
    load => write_reg2,
    Clk => Clk,
    Q => reg2_q

```

```

);
-- register 3
reg03: reg16 PORT MAP(
    D => d_data,
    load => write_reg3,
    Clk => Clk,
    Q => reg3_q
);
-- register 4
reg04: reg16 PORT MAP(
    D => d_data,
    load => write_reg4,
    Clk => Clk,
    Q => reg4_q
);
-- register 5
reg05: reg16 PORT MAP(
    D => d_data,
    load => write_reg5,
    Clk => Clk,
    Q => reg5_q
);
-- register 6
reg06: reg16 PORT MAP(
    D => d_data,
    load => write_reg6,
    Clk => Clk,
    Q => reg6_q
);

```

```

-- register 7
reg07: reg16 PORT MAP(
    D => d_data,
    load => write_reg7,
    Clk => Clk,
    Q => reg7_q
);

-- register 8
reg08: reg16 PORT MAP(
    D => d_data,
    load => write_reg8,
    Clk => Clk,
    Q => reg8_q
);

-- Destination register decoder
des_decoder_4to16: decoder_4to16 PORT MAP(
    A0 => des_sel(0),
    A1 => des_sel(1),
    A2 => des_sel(2),
    A3 => TD,
    Q0 => load_reg0,
    Q1 => load_reg1,
    Q2 => load_reg2,
    Q3 => load_reg3,
    Q4 => load_reg4,
    Q5 => load_reg5,
    Q6 => load_reg6,
    Q7 => load_reg7,

```

```

    Q8 => load_reg8,
    Q9 => load_reg9,
    Q10 => load_reg10,
    Q11 => load_reg11,
    Q12 => load_reg12,
    Q13 => load_reg13,
    Q14 => load_reg14,
    Q15 => load_reg15
);

-- 16 to 1 source register multiplexer
a_data_mux: mux16_16bit PORT MAP(
    In0 => reg0_q,
    In1 => reg1_q,
    In2 => reg2_q,
    In3 => reg3_q,
    In4 => reg4_q,
    In5 => reg5_q,
    In6 => reg6_q,
    In7 => reg7_q,
    In8 => reg8_q,
    In9 => reg9_q,
    In10 => reg10_q,
    In11 => reg11_q,
    In12 => reg12_q,
    In13 => reg13_q,
    In14 => reg14_q,
    In15 => reg15_q,

```

```

    S0 => a_sel(0),
    S1 => a_sel(1),
    S2 => a_sel(2),
    S3 => TA,
    Z => a_data
);

-- 16 to 1 source register multiplexer
b_data_mux: mux16_16bit PORT MAP(
    In0 => reg0_q,
    In1 => reg1_q,
    In2 => reg2_q,
    In3 => reg3_q,
    In4 => reg4_q,
    In5 => reg5_q,
    In6 => reg6_q,
    In7 => reg7_q,
    In8 => reg8_q,
    In9 => reg9_q,
    In10 => reg10_q,
    In11 => reg11_q,
    In12 => reg12_q,
    In13 => reg13_q,
    In14 => reg14_q,
    In15 => reg15_q,
    S0 => b_sel(0),
    S1 => b_sel(1),
    S2 => b_sel(2),
    S3 => TB,

```

```

Z => b_data

);

write_reg0 <= (load_reg0 and load_enable) or reset;
write_reg1 <= (load_reg1 and load_enable) or reset;
write_reg2 <= (load_reg2 and load_enable) or reset;
write_reg3 <= (load_reg3 and load_enable) or reset;
write_reg4 <= (load_reg4 and load_enable) or reset;
write_reg5 <= (load_reg5 and load_enable) or reset;
write_reg6 <= (load_reg6 and load_enable) or reset;
write_reg7 <= (load_reg7 and load_enable) or reset;
write_reg8 <= (TD and load_enable) or reset;
write_reg9 <= (load_reg9 and load_enable) or reset;
write_reg10 <= (load_reg10 and load_enable) or reset;
write_reg11 <= (load_reg11 and load_enable) or reset;
write_reg12 <= (load_reg12 and load_enable) or reset;
write_reg13 <= (load_reg13 and load_enable) or reset;
write_reg14 <= (load_reg14 and load_enable) or reset;
write_reg15 <= (load_reg15 and load_enable) or reset;

d_data <= x"0000" when reset='1' else input_data;

```

```
end Behavioral;
```

2.16 LOGIC CIRCUIT

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```



```
-- USE ieee.numeric_std.ALL;
```

```
entity logic_circuit_16bit is
```

```
Port (
```

```
A: in STD_LOGIC_VECTOR(15 downto 0);
```

```
B: in STD_LOGIC_VECTOR(15 downto 0);
```

```
s0,s1: in STD_LOGIC;
```

```
Y: out STD_LOGIC_VECTOR(15 downto 0));
```

```
end logic_circuit_16bit;
```

```
architecture Behavioral of logic_circuit_16bit is
```

```
COMPONENT mux4_16bits
```

```
Port(
```

```
In0, In1, In2, In3: in std_logic_vector(15 downto 0);
```

```
S0, S1 : in std_logic;
```

```
Z : out std_logic_vector(15 downto 0));
```

```
End Component;
```

```
signal sig1,sig2,sig3,sig4: std_logic_vector(15 downto 0);
```

```
begin
```

```
sig1(0) <= A(0) and B(0) after 1 ns;
```

```
sig1(1) <= A(1) and B(1) after 1 ns;
```

```
sig1(2) <= A(2) and B(2) after 1 ns;
```

```
sig1(3) <= A(3) and B(3) after 1 ns;
```

```
sig1(4) <= A(4) and B(4) after 1 ns;
```

```
sig1(5) <= A(5) and B(5) after 1 ns;
```

```
sig1(6) <= A(6) and B(6) after 1 ns;
```

sig1(7) <= A(7) and B(7) after 1 ns;
sig1(8) <= A(8) and B(8) after 1 ns;
sig1(9) <= A(9) and B(9) after 1 ns;
sig1(10) <=A(10) and B(10) after 1 ns;
sig1(11) <=A(11) and B(11) after 1 ns;
sig1(12) <=A(12) and B(12) after 1 ns;
sig1(13) <=A(13) and B(13) after 1 ns;
sig1(14) <=A(14) and B(14) after 1 ns;
sig1(15) <=A(15) and B(15) after 1 ns;
--sig1(8) <= ln0(8) and ln1(8) after 1 ns;

sig2(0) <= A(0) or B(0) after 1 ns;
sig2(1) <= A(1) or B(1) after 1 ns;
sig2(2) <= A(2) or B(2) after 1 ns;
sig2(3) <= A(3) or B(3) after 1 ns;
sig2(4) <= A(4) or B(4) after 1 ns;
sig2(5) <= A(5) or B(5) after 1 ns;
sig2(6) <= A(6) or B(6) after 1 ns;
sig2(7) <= A(7) or B(7) after 1 ns;
sig2(8) <= A(8) or B(8) after 1 ns;
sig2(9) <= A(9) or B(9) after 1 ns;
sig2(10) <=A(10)or B(10) after 1 ns;
sig2(11) <=A(11)or B(11) after 1 ns;
sig2(12) <=A(12)or B(12) after 1 ns;
sig2(13) <=A(13)or B(13) after 1 ns;
sig2(14) <=A(14)or B(14) after 1 ns;
sig2(15) <=A(15)or B(15) after 1 ns;

sig3(0) <= A(0) xor B(0) after 1 ns;
sig3(1) <= A(1) xor B(1) after 1 ns;
sig3(2) <= A(2) xor B(2) after 1 ns;
sig3(3) <= A(3) xor B(3) after 1 ns;
sig3(4) <= A(4) xor B(4) after 1 ns;
sig3(5) <= A(5) xor B(5) after 1 ns;
sig3(6) <= A(6) xor B(6) after 1 ns;
sig3(7) <= A(7) xor B(7) after 1 ns;
sig3(8) <= A(8) xor B(8) after 1 ns;
sig3(9) <= A(9) xor B(9) after 1 ns;
sig3(10) <=A(10) xor B(10) after 1 ns;
sig3(11) <=A(11) xor B(11) after 1 ns;
sig3(12) <=A(12) xor B(12) after 1 ns;
sig3(13) <=A(13) xor B(13) after 1 ns;
sig3(14) <=A(14) xor B(14) after 1 ns;
sig3(15) <=A(15) xor B(15) after 1 ns;

sig4(0) <= not A(0) after 1 ns;
sig4(1) <= not A(1) after 1 ns;
sig4(2) <= not A(2) after 1 ns;
sig4(3) <= not A(3) after 1 ns;
sig4(4) <= not A(4) after 1 ns;
sig4(5) <= not A(5) after 1 ns;
sig4(6) <= not A(6) after 1 ns;
sig4(7) <= not A(7) after 1 ns;
sig4(8) <= not A(8) after 1 ns;
sig4(9) <= not A(9) after 1 ns;
sig4(10) <=not A(10) after 1 ns;

```

sig4(11) <=not A(11) after 1 ns;
sig4(12) <=not A(12) after 1 ns;
sig4(13) <=not A(13) after 1 ns;
sig4(14) <=not A(14) after 1 ns;
sig4(15) <=not A(15) after 1 ns;

```

```

mux4_16bit : mux4_16bits PORT MAP(
S0 => s0,
S1 => s1,
In0 => sig1,
In1 => sig2,
In2 => sig3,
In3 => sig4,
Z => Y
);

```

```

end Behavioral;

```

2.17 DATAPATH

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

entity last_data_path is

```

```

    Port ( PC : in  STD_LOGIC_VECTOR (15 downto 0);
          data_in : in  STD_LOGIC_VECTOR (15 downto 0);

          DR : IN  std_logic_vector(2 downto 0);
          SA : IN  std_logic_vector(2 downto 0);
          SB : IN  std_logic_vector(2 downto 0);
          TD : IN  std_logic;
          TA : IN  std_logic;

```

```

TB : IN std_logic;
Clk : in STD_LOGIC;
    reset : OUT STD_LOGIC;
FS : IN std_logic_vector(4 downto 0);
RW : IN std_logic;
MB : IN std_logic;
MM : IN std_logic;
MD : IN std_logic;
data_out : out STD_LOGIC_VECTOR (15 downto 0);
address_out : out STD_LOGIC_VECTOR (15 downto 0);
V : out STD_LOGIC;
C : out STD_LOGIC;
N : out STD_LOGIC;
Z : out STD_LOGIC);
end last_data_path;

```

architecture Behavioral of last_data_path is

```

COMPONENT new_reg_file_9x16bit
PORT(
    des_sel : IN std_logic_vector(2 downto 0);
    a_sel : IN std_logic_vector(2 downto 0);
    b_sel : IN std_logic_vector(2 downto 0);
        TD : IN std_logic;
        TA : IN std_logic;
        TB : IN std_logic;
    load_enable : IN std_logic;
        reset : in std_logic;
    Clk : IN std_logic;

```

```

    input_data : IN std_logic_vector(15 downto 0);
    a_data : OUT std_logic_vector(15 downto 0);
    b_data : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;

COMPONENT zero_fill
PORT(
    SB : IN std_logic_vector(2 downto 0);
    constant_out : out std_logic_vector(15 downto 0)
);
END COMPONENT;

COMPONENT functional_unit_16bit
PORT(
    FSS : IN std_logic_vector(4 downto 0);
    A : IN std_logic_vector(15 downto 0);
    B : IN std_logic_vector(15 downto 0);
    F : OUT std_logic_vector(15 downto 0);
    V : OUT std_logic;
    C : OUT std_logic;
    N : OUT std_logic;
    Z : OUT std_logic
);
END COMPONENT;

COMPONENT mux_2_16bit
PORT(
    S : IN std_logic;

```

```

In0 : IN std_logic_vector(15 downto 0);
In1 : IN std_logic_vector(15 downto 0);
Z : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;

```

```

--signals

signal Cout : std_logic;
signal Vout : std_logic;
signal reset1 : std_logic := '0';
signal mux_b_out : std_logic_vector(15 downto 0);
signal mux_d_out : std_logic_vector(15 downto 0);
signal zero_fill_out : std_logic_vector(15 downto 0);
signal functional_unit_out : std_logic_vector(15 downto 0);
signal d_data : std_logic_vector(15 downto 0);
signal a_reg_file_out : std_logic_vector(15 downto 0);
signal b_reg_file_out : std_logic_vector(15 downto 0);

begin

reg_file: new_reg_file_9x16bit PORT MAP (
    des_sel(2 downto 0) => DR,
        TD => TD,
    a_sel(2 downto 0) => SA,
        TA => TA,
    b_sel(2 downto 0) => SB,
        TB => TB,
    load_enable => RW,
        reset => reset1,

```

```

-- reset => reset,
--reset1 => reset,
Clk => Clk,
input_data => mux_d_out,
a_data => a_reg_file_out,
b_data => b_reg_file_out
);

```

```

z_fill: zero_fill PORT MAP (
    SB => SB,
    constant_out => zero_fill_out
);

```

```

func_unit: functional_unit_16bit PORT MAP (
    FSS => FS,
    A => a_reg_file_out,
    B => mux_b_out,
    F => functional_unit_out,
    V => V,
    C => C,
    N => N,
    Z => Z
);

```

```

mux_b: mux_2_16bit PORT MAP (
    S => MB,
    In0 => b_reg_file_out,
    In1 => zero_fill_out,
    Z => mux_b_out
);

```



```
);
```

```
mux_d: mux_2_16bit PORT MAP (
```

```
    S => MD,
```

```
    In0 => functional_unit_out,
```

```
    In1 => data_in,
```

```
    Z => mux_d_out
```

```
);
```

```
mux_m: mux_2_16bit PORT MAP (
```

```
    S => MM,
```

```
    In0 => a_reg_file_out,
```

```
    In1 => PC,
```

```
    Z => address_out
```

```
);
```

```
reset <= reset1;
```

```
data_out <= mux_b_out;
```

```
end Behavioral;
```

2.18 DECODER3_8

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.STD_LOGIC_ARITH.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity decoder_3to8 is
```

```
    Port ( A0 : in  STD_LOGIC;
```

```
          A1 : in  STD_LOGIC;
```

```
          A2 : in  STD_LOGIC;
```

```
          Q0 : out STD_LOGIC;
```

```

    Q1 : out STD_LOGIC;
    Q2 : out STD_LOGIC;
    Q3 : out STD_LOGIC;
    Q4 : out STD_LOGIC;
    Q5 : out STD_LOGIC;
    Q6 : out STD_LOGIC;
    Q7 : out STD_LOGIC);
end decoder_3to8;

```

architecture Behavioral of decoder_3to8 is

```

begin
Q0 <= ( (not A0) and (not A1) and (not A2) ) after 5 ns;
Q1 <= ( A0 and (not A1) and (not A2) ) after 5 ns;
Q2 <= ( (not A0) and A1 and (not A2) ) after 5 ns;
Q3 <= ( A0 and A1 and (not A2) ) after 5 ns;
Q4 <= ( (not A0) and (not A1) and A2 ) after 5 ns;
Q5 <= ( A0 and (not A1) and A2 ) after 5 ns;
Q6 <= ( (not A0) and A1 and A2 ) after 5 ns;
Q7 <= ( A0 and A1 and A2 ) after 5 ns;
end Behavioral;

```

2.19 DECODER4_16

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

entity decoder_4to16 is

```

    Port ( A0 : in STD_LOGIC;
          A1 : in STD_LOGIC;

```

```

    A2 : in STD_LOGIC;
    A3 : in STD_LOGIC;
    Q0 : out STD_LOGIC;
    Q1 : out STD_LOGIC;
    Q2 : out STD_LOGIC;
    Q3 : out STD_LOGIC;
    Q4 : out STD_LOGIC;
    Q5 : out STD_LOGIC;
    Q6 : out STD_LOGIC;
    Q7 : out STD_LOGIC;
    Q8 : out STD_LOGIC;
    Q9 : out STD_LOGIC;
    Q10 : out STD_LOGIC;
    Q11 : out STD_LOGIC;
    Q12 : out STD_LOGIC;
    Q13 : out STD_LOGIC;
    Q14 : out STD_LOGIC;
    Q15 : out STD_LOGIC);
end decoder_4to16;

```

architecture Behavioral of decoder_4to16 is

```

begin
    Q0 <= ( (not A0) and (not A1) and (not A2) and (not A3) );
    Q1 <= ( A0 and (not A1) and (not A2) and (not A3));
    Q2 <= ( (not A0) and A1 and (not A2) and (not A3));
    Q3 <= ( A0 and A1 and (not A2) and (not A3));
    Q4 <= ( (not A0) and (not A1) and A2 and (not A3));
    Q5 <= ( A0 and (not A1) and A2 and (not A3));

```

```

Q6 <= ( (not A0) and A1 and A2 and (not A3));
Q7 <= ( A0 and A1 and A2 and (not A3));
Q8 <= ( (not A0) and (not A1) and (not A2) and A3);
Q9 <= ( A0 and (not A1) and (not A2) and A3);
Q10 <= ( (not A0) and A1 and (not A2) and A3);
Q11 <= ( A0 and A1 and (not A2) and A3);
Q12 <= ( (not A0) and (not A1) and A2 and A3);
Q13 <= ( A0 and (not A1) and A2 and A3);
Q14 <= ( (not A0) and A1 and A2 and A3);
Q15 <= ( A0 and A1 and A2 and A3);
end Behavioral;

```

2.20 MUX16_16BIT

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

```

entity mux16_16bit is

```

    Port ( S0 : in STD_LOGIC;
           S1 : in STD_LOGIC;
           S2 : in STD_LOGIC;
           S3 : in STD_LOGIC;
           In0 : in STD_LOGIC_VECTOR (15 downto 0);
           In1 : in STD_LOGIC_VECTOR (15 downto 0);
           In2 : in STD_LOGIC_VECTOR (15 downto 0);
           In3 : in STD_LOGIC_VECTOR (15 downto 0);
           In4 : in STD_LOGIC_VECTOR (15 downto 0);
           In5 : in STD_LOGIC_VECTOR (15 downto 0);
           In6 : in STD_LOGIC_VECTOR (15 downto 0);
           In7 : in STD_LOGIC_VECTOR (15 downto 0);

```

```

    In8 : in STD_LOGIC_VECTOR (15 downto 0);
    In9 : in STD_LOGIC_VECTOR (15 downto 0);
    In10 : in STD_LOGIC_VECTOR (15 downto 0);
    In11 : in STD_LOGIC_VECTOR (15 downto 0);
    In12 : in STD_LOGIC_VECTOR (15 downto 0);
    In13 : in STD_LOGIC_VECTOR (15 downto 0);
    In14 : in STD_LOGIC_VECTOR (15 downto 0);
    In15 : in STD_LOGIC_VECTOR (15 downto 0);
    Z : out STD_LOGIC_VECTOR (15 downto 0));
end mux16_16bit;

```

architecture Behavioral of mux16_16bit is

```

begin
Z <= In0 when (S0='0' and S1='0' and S2='0' and S3='0') else
In1 when (S0='1' and S1='0' and S2='0' and S3='0') else
In2 when (S0='0' and S1='1' and S2='0' and S3='0') else
In3 when (S0='1' and S1='1' and S2='0' and S3='0') else
In4 when (S0='0' and S1='0' and S2='1' and S3='0') else
In5 when (S0='1' and S1='0' and S2='1' and S3='0') else
In6 when (S0='0' and S1='1' and S2='1' and S3='0') else
In7 when (S0='1' and S1='1' and S2='1' and S3='0') else
In8 when (S0='0' and S1='0' and S2='0' and S3='1') else
In9 when (S0='1' and S1='0' and S2='0' and S3='1') else
In10 when (S0='0' and S1='1' and S2='0' and S3='1') else
In11 when (S0='1' and S1='1' and S2='0' and S3='1') else
In12 when (S0='0' and S1='0' and S2='1' and S3='1') else
In13 when (S0='1' and S1='0' and S2='1' and S3='1') else
In14 when (S0='0' and S1='1' and S2='1' and S3='1') else

```

```

In15 when (S0='1' and S1='1' and S2='1' and S3='1') else
x"0000";
end Behavioral;

```

2.21 MUX16_1BIT

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

entity mux16_1bit is

```

    Port ( S0 : in  STD_LOGIC;
           S1 : in  STD_LOGIC;
           S2 : in  STD_LOGIC;
           S3 : in  STD_LOGIC;
           A : in  STD_LOGIC_VECTOR (15 downto 0);
           F : out STD_LOGIC);

```

end mux16_1bit;

architecture Behavioral of mux16_1bit is

begin

```

F <= A(0) when (S3='0' and S2='0' and S1='0' and S0='0') else
A(1) when (S3='0' and S2='0' and S1='0' and S0='1') else
A(2) when (S3='0' and S2='0' and S1='1' and S0='0') else
A(3) when (S3='0' and S2='0' and S1='1' and S0='1') else
A(4) when (S3='0' and S2='1' and S1='0' and S0='0') else
A(5) when (S3='0' and S2='1' and S1='0' and S0='1') else
A(6) when (S3='0' and S2='1' and S1='1' and S0='0') else
A(7) when (S3='0' and S2='1' and S1='1' and S0='1') else
A(8) when (S3='1' and S2='0' and S1='0' and S0='0') else
A(9) when (S3='1' and S2='0' and S1='0' and S0='1') else

```

```

A(10) when (S3='1' and S2='0' and S1='1' and S0='0') else
A(11) when (S3='1' and S2='0' and S1='1' and S0='1') else
A(12) when (S3='1' and S2='1' and S1='0' and S0='0') else
A(13) when (S3='1' and S2='1' and S1='0' and S0='1') else
A(14) when (S3='1' and S2='1' and S1='1' and S0='0') else
A(15) when (S3='1' and S2='1' and S1='1' and S0='1');
end Behavioral;

```

2.22 MUX2_16BIT

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity mux_2_16bit is
    Port ( S : in STD_LOGIC;
          In0 : in STD_LOGIC_VECTOR (15 downto 0);
          In1 : in STD_LOGIC_VECTOR (15 downto 0);
          Z : out STD_LOGIC_VECTOR (15 downto 0));
end mux_2_16bit;

```

architecture Behavioral of mux_2_16bit is

```

begin

Z <= In0 when S='0' else
In1 when S='1' else
x"0000";

end Behavioral;

```

2.23 MUX2_8BIT

```

library IEEE;

```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity mux_2_to_1_8bit is
```

```
    Port ( In0 : in  STD_LOGIC_VECTOR (7 downto 0);
```

```
          In1 : in  STD_LOGIC_VECTOR (7 downto 0);
```

```
          S : in STD_LOGIC;
```

```
          Z : out STD_LOGIC_VECTOR (7 downto 0));
```

```
end mux_2_to_1_8bit;
```

```
architecture Behavioral of mux_2_to_1_8bit is
```

```
begin
```

```
    Z <= In0 when S='0' else
```

```
    In1 when S='1' else
```

```
    x"00";
```

```
end Behavioral;
```

2.24 MUX8_16BIT

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity mux8_16bit is
```

```
    Port ( S0 : in  STD_LOGIC;
```

```
          S1 : in  STD_LOGIC;
```

```
          S2 : in  STD_LOGIC;
```

```
          In0 : in  STD_LOGIC_VECTOR (15 downto 0);
```

```
          In1 : in  STD_LOGIC_VECTOR (15 downto 0);
```

```
          In2 : in  STD_LOGIC_VECTOR (15 downto 0);
```



```

    In3 : in STD_LOGIC_VECTOR (15 downto 0);
    In4 : in STD_LOGIC_VECTOR (15 downto 0);
    In5 : in STD_LOGIC_VECTOR (15 downto 0);
    In6 : in STD_LOGIC_VECTOR (15 downto 0);
    In7 : in STD_LOGIC_VECTOR (15 downto 0);
    Z : out STD_LOGIC_VECTOR (15 downto 0));
end mux8_16bit;

```

architecture Behavioral of mux8_16bit is

```

begin
Z <= In0 when (S0='0' and S1='0' and S2='0') else
In1 when (S0='1' and S1='0' and S2='0') else
In2 when (S0='0' and S1='1' and S2='0') else
In3 when (S0='1' and S1='1' and S2='0') else
In4 when (S0='0' and S1='0' and S2='1') else
In5 when (S0='1' and S1='0' and S2='1') else
In6 when (S0='0' and S1='1' and S2='1') else
In7 when (S0='1' and S1='1' and S2='1') else
x"0000";
end Behavioral;

```

2.25 MUX8_1BIT

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

entity mux_8_to_1_1bit is

```

    Port ( A : in STD_LOGIC_VECTOR (7 downto 0);
          S0 : in STD_LOGIC;

```

```

        S1 : in STD_LOGIC;
        S2 : in STD_LOGIC;
        line_out : out STD_LOGIC);
end mux_8_to_1_1bit;

```

architecture Behavioral of mux_8_to_1_1bit is

```

begin
line_out <= A(0) when (S2='0' and S1='0' and S0='0') else
A(1) when (S2='0' and S1='0' and S0='1') else
A(2) when (S2='0' and S1='1' and S0='0') else
A(3) when (S2='0' and S1='1' and S0='1') else
A(4) when (S2='1' and S1='0' and S0='0') else
A(5) when (S2='1' and S1='0' and S0='1') else
A(6) when (S2='1' and S1='1' and S0='0') else
A(7) when (S2='1' and S1='1' and S0='1') else '0';

end Behavioral;

```

2.26 FULL ADDER

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

entity full_adder is

```

    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          Cin : in STD_LOGIC;
          S : out STD_LOGIC;
          Cout : out STD_LOGIC);

```

```
end full_adder;
```

architecture Behavioral of full_adder is

```
begin
```

```
S <= ((A xor B) xor Cin);
```

```
Cout <= ((Cin and (A xor B)) or (A and B));
```

```
end Behavioral;
```

2.27 MUXB_Y_16BIT

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

entity b_to_y_16bit is

```
    Port ( B : in  STD_LOGIC_VECTOR (15 downto 0);
```

```
          Y : out  STD_LOGIC_VECTOR (15 downto 0);
```

```
          S0 : in  std_logic;
```

```
          S1 : in  std_logic
```

```
          );
```

```
end b_to_y_16bit;
```

architecture Behavioral of b_to_y_16bit is

```
begin
```

```
Y <= x"0000" when (S0='0' and S1='0') else
```

```
B when (S0='1' and S1='0') else
```

```
(not B) when (S0='0' and S1='1') else
```

```
x"FFFF" when (S0='1' and S1='1');
```

```
end Behavioral;
```

2.28 REGISTER

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity reg16 is

Port (D : in STD_LOGIC_VECTOR (15 downto 0);

load : in STD_LOGIC;

Clk : in STD_LOGIC;

Q : out STD_LOGIC_VECTOR (15 downto 0));

end reg16;

architecture Behavioral of reg16 is

begin

process(Clk)

begin

if (rising_edge(Clk)) then

if load='1' then

Q<=D;

end if;

end if;

end process;

end Behavioral;

3.

3.1 PROCESSOR FINAL

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

ENTITY processor_final_TestBench IS

```
END processor_final_TestBench;
```

```
ARCHITECTURE behavior OF processor_final_TestBench IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT processor_final
```

```
PORT(
```

```
    Clk : IN std_logic;
```

```
    reset : IN std_logic
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal Clk : std_logic := '0';
```

```
signal reset : std_logic := '0';
```

```
-- Clock period definitions
```

```
constant Clk_period : time := 10 ns;
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
 uut: Processor_final PORT MAP (
```

```
    Clk => Clk,
```

```
    reset => reset
```

```
);
```

-- Clock process definitions

Clk_process :process

begin

 Clk <= '0';

 wait for Clk_period/2;

 Clk <= '1';

 wait for Clk_period/2;

end process;

-- Stimulus process

stim_proc: process

begin

 reset <= '1';

 wait for 100 ns;

 reset <= '0';

 wait;

end process;

END;

3.2 ARITHMETIC LOGICAL UNIT

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

ENTITY ALU_unit_16bit_TestBench IS

END ALU_unit_16bit_TestBench;

ARCHITECTURE behavior OF ALU_unit_16bit_TestBench IS

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT ALU_unit_16bit

PORT(

A : IN std_logic_vector(15 downto 0);

B : IN std_logic_vector(15 downto 0);

Cin : in STD_LOGIC;

S0 : IN std_logic;

S1 : IN std_logic;

S2 : IN std_logic;

Cout : OUT std_logic;

Vout : OUT std_logic;

G : OUT std_logic_vector(15 downto 0)

);

END COMPONENT;

--Inputs

signal A : std_logic_vector(15 downto 0) := (others => '0');

signal B : std_logic_vector(15 downto 0) := (others => '0');

signal Cin : std_logic := '0';

signal S0 : std_logic := '0';

signal S1 : std_logic := '0';

signal S2 : std_logic := '0';

--Outputs

signal Cout : std_logic;

signal Vout : std_logic;

signal G : std_logic_vector(15 downto 0);

```
-- No clocks detected in port list. Replace <clock> below with  
-- appropriate port name
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: ALU_unit_16bit PORT MAP (
```

```
    A => A,
```

```
    B => B,
```

```
        Cin => Cin,
```

```
    S0 => S0,
```

```
    S1 => S1,
```

```
    S2 => S2,
```

```
    Cout => Cout,
```

```
    Vout => Vout,
```

```
    G => G
```

```
);
```

```
--CYCLE TROUGH DIFFERENT INPUTS
```

```
-- TO TEST EACH OPERATION
```

```
stim_proc1: process
```

```
begin
```

```
    wait for 50 ns;
```

```
        S0 <= not S0;
```

```
end process;
```

```
stim_proc2: process
```

```
begin
```



```
    wait for 100 ns;
        S1 <= not S1;
end process;
```

```
stim_proc3: process
begin
    wait for 200 ns;
        S2 <= not S2;
end process;
```

```
stim_proc4: process
begin
    A <= x"00FA";
    B <= x"002A";
    wait for 400 ns;
end process;
```

```
END;
```

3.3 CONTROL ADDRESS REGISTER

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY CAR_TestBench IS
```

```
END CAR_TestBench;
```

```
ARCHITECTURE behavior OF CAR_TestBench IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

COMPONENT CAR

PORT(

data_in : IN std_logic_vector(7 downto 0);

reset : IN std_logic;

Clk : IN std_logic;

Con : IN std_logic;

data_out : OUT std_logic_vector(7 downto 0)

);

END COMPONENT;

--Inputs

signal data_in : std_logic_vector(7 downto 0) := (others => '0');

signal Con : std_logic := '0';

signal Clk : std_logic := '0';

signal reset : std_logic := '0';

--Outputs

signal data_out : std_logic_vector(7 downto 0);

-- Clock period definitions

constant Clk_period : time := 10 ns;

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: CAR PORT MAP (

data_in => data_in,

reset => reset,

```

        Clk => Clk,

        Con => Con,

        data_out => data_out

    );

-- Clock process definitions

Clk_process :process

begin

    Clk <= '0';

    wait for Clk_period/2;

    Clk <= '1';

    wait for Clk_period/2;

end process;


-- Stimulus process

stim_proc0: process

begin

    --Load the CAR with the input (condition == 1)

    data_in <= "01000001";

    Con <= '1';

    reset <='0';

    --data_out = 01000001

    wait for Clk_period*2;


    --Increment the CAR (condition == 0)

    data_in <= "01000001";

    Con <= '0';

    --data_out = 01000010

    wait;

```

```
end process;
```

```
END;
```

3.4 EXTEND

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY Extend_TestBench IS
```

```
END Extend_TestBench;
```

```
ARCHITECTURE behavior OF Extend_TestBench IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT Extend
```

```
PORT(
```

```
    DR : IN  std_logic_vector(2 downto 0);
```

```
    SB : IN  std_logic_vector(2 downto 0);
```

```
    extension : OUT std_logic_vector(15 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal DR : std_logic_vector(2 downto 0) := (others => '0');
```

```
signal SB : std_logic_vector(2 downto 0) := (others => '0');
```

```
--Outputs
```

```
signal extension : std_logic_vector(15 downto 0);
```

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: Extend PORT MAP (

DR => DR,

SB => SB,

extension => extension

);

-- Stimulus process

stim_proc: process

begin

-- Test with most significant bit = 1

DR <= "101";

SB <= "010";

-- Extension = 111111111101010

wait for 100 ns;

-- Test with most significant bit = 0

DR <= "011";

SB <= "011";

-- Extension = 000000000011011

wait;

end process;

END;

3.5 INSTRUCTION REGISTER

LIBRARY ieee;

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY IR_TestBench IS
```

```
END IR_TestBench;
```

```
ARCHITECTURE behavior OF IR_TestBench IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT IR
```

```
PORT(
```

```
    data_in : IN std_logic_vector(15 downto 0);
```

```
    IL : IN std_logic;
```

```
        Clk : IN std_logic;
```

```
    Opcode : OUT std_logic_vector(6 downto 0);
```

```
    DR : OUT std_logic_vector(2 downto 0);
```

```
    SA : OUT std_logic_vector(2 downto 0);
```

```
    SB : OUT std_logic_vector(2 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal data_in : std_logic_vector(15 downto 0) := (others => '0');
```

```
signal IL : std_logic := '0';
```

```
signal Clk : std_logic := '0';
```

```
--Outputs
```

```
signal Opcode : std_logic_vector(6 downto 0);
```

```
signal DR : std_logic_vector(2 downto 0);  
signal SA : std_logic_vector(2 downto 0);  
signal SB : std_logic_vector(2 downto 0);
```

```
-- Clock period definitions
```

```
constant Clk_period : time := 10 ns;
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: IR PORT MAP (
```

```
    data_in => data_in,
```

```
    IL => IL,
```

```
        Clk => Clk,
```

```
    Opcode => Opcode,
```

```
    DR => DR,
```

```
    SA => SA,
```

```
    SB => SB
```

```
);
```

```
-- Clock process definitions
```

```
Clk_process :process
```

```
begin
```

```
    Clk <= '0';
```

```
    wait for Clk_period/2;
```

```
    Clk <= '1';
```

```
    wait for Clk_period/2;
```

```
end process;
```

```

-- Stimulus process
stim_proc0: process
begin
    --Test Data being loaded in.
    --Opcode = 0100000, DR = 111, SA = 101, SB = 011.
    --Data in = 0100000 111 101 011, IL = 1.
    data_in <= "0100000111101011";
    IL <= '1';
    wait for Clk_period*2;

    --Test Data not being loaded in. (Therefore the Outputs are the same as the
last test)
    --Opcode = 0100000, DR = 111, SA = 101, SB = 011.
    --Data in = 0011100 010 111 000, IL = 1.
    data_in <= "0011100010111000";
    IL <= '0';
    wait;

end process;

END;

```

3.6 MICROPROGRAMMED CONTROL

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Microprogrammed_control_TestBench IS
END Microprogrammed_control_TestBench;

ARCHITECTURE behavior OF Microprogrammed_control_TestBench IS

```


-- Component Declaration for the Unit Under Test (UUT)

COMPONENT Microprogrammed_control

PORT(

instruction_in : IN std_logic_vector(15 downto 0);

reset : IN std_logic;

V : IN std_logic;

C : IN std_logic;

N : IN std_logic;

Z : IN std_logic;

Clk : IN std_logic;

pc_out : OUT std_logic_vector(15 downto 0);

DR : OUT std_logic_vector(2 downto 0);

SA : OUT std_logic_vector(2 downto 0);

SB : OUT std_logic_vector(2 downto 0);

TD : OUT std_logic;

TA : OUT std_logic;

TB : OUT std_logic;

MB : OUT std_logic;

FS : OUT std_logic_vector(4 downto 0);

MD : OUT std_logic;

RW : OUT std_logic;

MM : OUT std_logic;

MW : OUT std_logic

);

END COMPONENT;

--Inputs

```
signal instruction_in : std_logic_vector(15 downto 0) := (others => '0');  
signal reset : std_logic := '0';  
signal V : std_logic := '0';  
signal C : std_logic := '0';  
signal N : std_logic := '0';  
signal Z : std_logic := '0';  
signal Clk : std_logic := '0';
```

--Outputs

```
signal pc_out : std_logic_vector(15 downto 0);  
signal DR : std_logic_vector(2 downto 0);  
signal SA : std_logic_vector(2 downto 0);  
signal SB : std_logic_vector(2 downto 0);  
signal TD : std_logic;  
signal TA : std_logic;  
signal TB : std_logic;  
signal MB : std_logic;  
signal FS : std_logic_vector(4 downto 0);  
signal MD : std_logic;  
signal RW : std_logic;  
signal MM : std_logic;  
signal MW : std_logic;
```

-- Clock period definitions

```
constant Clk_period : time := 10 ns;
```

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: Microprogrammed_control PORT MAP (

instruction_in => instruction_in,

reset => reset,

V => V,

C => C,

N => N,

Z => Z,

Clk => Clk,

pc_out => pc_out,

DR => DR,

SA => SA,

SB => SB,

TD => TD,

TA => TA,

TB => TB,

MB => MB,

FS => FS,

MD => MD,

RW => RW,

MM => MM,

MW => MW

);

-- Clock process definitions

Clk_process :process

begin

Clk <= '0';

wait for Clk_period/2;

Clk <= '1';

```
        wait for Clk_period/2;
end process;
```

```
stim_proc: process
```

```
begin
```

```
    reset <= '1';
```

```
    wait for 20 ns;
```

```
    -- Testing instruction = 1101001000110111
```

```
    reset <= '0';
```

```
    instruction_in <= x"D237";
```

```
    -- output should be
```

```
    -- pc 0000000000000001
```

```
    -- dr 000
```

```
    -- sa 110
```

```
    -- sb 111
```

```
    -- td 0
```

```
    -- ta 0
```

```
    -- tb 0
```

```
    -- mb 0
```

```
    -- fs 00000
```

```
    -- md 0
```

```
    -- rw 0
```

```
    -- mm 0
```

```
    -- mw 0
```

```
wait;
```

```
end process;
```

```
END;
```

3.7 PROGRAM COUNTER

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY PC_TestBench IS
```

```
END PC_TestBench;
```

```
ARCHITECTURE behavior OF PC_TestBench IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT PC
```

```
PORT(
```

```
    Extend : IN std_logic_vector(15 downto 0);
```

```
        reset : IN std_logic;
```

```
        Clk : IN std_logic;
```

```
    PL : IN std_logic;
```

```
    PI : IN std_logic;
```

```
    PC_out : OUT std_logic_vector(15 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal Extend : std_logic_vector(15 downto 0) := (others => '0');
```

```
signal PL : std_logic := '0';
```

```

signal PI : std_logic := '0';

signal reset : std_logic := '0';

signal Clk : std_logic := '0';


--Outputs

signal PC_out : std_logic_vector(15 downto 0);


-- Clock period definitions

constant Clk_period : time := 10 ns;


BEGIN


    -- Instantiate the Unit Under Test (UUT)

    uut: PC PORT MAP (
        Extend => Extend,
            reset => reset,
            Clk => Clk,

        PL => PL,
        PI => PI,
        PC_out => PC_out
    );


-- Clock process definitions

Clk_process :process
begin
    Clk <= '0';

    wait for Clk_period/2;

```

```
        Clk <= '1';  
        wait for Clk_period/2;  
end process;
```

```
-- Stimulus process
```

```
stim_proc0: process
```

```
begin
```

```
--Test reset
```

```
reset<='1';
```

```
Extend <= x"0005";
```

```
PI <= '0';
```

```
PL <= '0';
```

```
-- PC_out = 0x0000
```

```
wait for Clk_period*2;
```

```
--Test with PI = '0' and PL = '0'
```

```
reset<='0';
```

```
Extend <= x"0005";
```

```
PI <= '0';
```

```
PL <= '0';
```

```
-- PC_out = 0x0000
```

```
wait for Clk_period*2;
```

```
--Test with PI = '1' and PL = '0'
```

```
Extend <= x"0005";
```

```
PI <= '1';
```

```
PL <= '0';
```

```
-- PC_out = 0x0001
```

```

        wait for Clk_period;

        --Test with PI = '0', PL = '1' and offset as 0x101
        Extend <= x"0005";

        PI <= '0';

        PL <= '1';

        -- PC_out = 0x06

        wait;

    end process;

END;

```

3.8 BARREL SHIFTER

```

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

ENTITY barrel_shifter_16bit_TestBench IS
END barrel_shifter_16bit_TestBench;

ARCHITECTURE behavior OF barrel_shifter_16bit_TestBench IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT barrel_shifter_16bit
    PORT(
        B : IN  std_logic_vector(15 downto 0);
        S0 : IN  std_logic;
        S1 : IN  std_logic;
        S2 : IN  std_logic;

```



```
S3 : IN std_logic;  
F : OUT std_logic_vector(15 downto 0)  
);  
END COMPONENT;
```

--Inputs

```
signal b : std_logic_vector(15 downto 0) := (others => '0');  
signal S0 : std_logic := '0';  
signal S1 : std_logic := '0';  
signal S2 : std_logic := '0';  
signal S3 : std_logic := '0';
```

--Outputs

```
signal F : std_logic_vector(15 downto 0);  
-- No clocks detected in port list. Replace <clock> below with  
-- appropriate port name
```

BEGIN

-- Instantiate the Unit Under Test (UUT)

```
uut: barrel_shifter_16bit PORT MAP (  
    B => B,  
    S0 => S0,  
    S1 => S1,  
    S2 => S2,  
    S3 => S3,  
    F => F  
);
```

```
-- Stimulus process  
stim_proc0: process  
begin  
    wait for 25 ns;  
    S0 <= not S0;  
end process;
```

```
stim_proc1: process  
begin  
    wait for 50 ns;  
    S1 <= not S1;  
end process;
```

```
stim_proc2: process  
begin  
    wait for 100 ns;  
    S2 <= not S2;  
end process;
```

```
stim_proc3: process  
begin  
    wait for 200 ns;  
    S3 <= not S3;  
end process;
```

```
stim_proc4: process  
begin  
    B <= x"8000";
```

```
wait for 400 ns;  
    B <= x"C000";  
wait for 400 ns;  
end process;
```

```
END;
```

3.9 CONTROL MEMORY

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY control_memory_TestBench IS
```

```
END control_memory_TestBench;
```

```
ARCHITECTURE behavior OF control_memory_TestBench IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT control_memory
```

```
PORT(  
    MW : OUT std_logic;
```

```
    MM : OUT std_logic;
```

```
    RW : OUT std_logic;
```

```
    MD : OUT std_logic;
```

```
    FS : OUT std_logic_vector(4 downto 0);
```

```
    MB : OUT std_logic;
```

```
    TB : OUT std_logic;
```

```
    TA : OUT std_logic;
```

```
    TD : OUT std_logic;
```

```
    PL : OUT std_logic;
```

```

    PI : OUT std_logic;
    IL : OUT std_logic;
    MC : OUT std_logic;
    MS : OUT std_logic_vector(2 downto 0);
    NA : OUT std_logic_vector(7 downto 0);
    IN_CAR : IN std_logic_vector(7 downto 0)
);
END COMPONENT;

--Inputs
signal IN_CAR : std_logic_vector(7 downto 0) := (others => '0');

--Outputs
signal MW : std_logic;
signal MM : std_logic;
signal RW : std_logic;
signal MD : std_logic;
signal FS : std_logic_vector(4 downto 0);
signal MB : std_logic;
signal TB : std_logic;
signal TA : std_logic;
signal TD : std_logic;
signal PL : std_logic;
signal PI : std_logic;
signal IL : std_logic;
signal MC : std_logic;
signal MS : std_logic_vector(2 downto 0);
signal NA : std_logic_vector(7 downto 0);

```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: control_memory PORT MAP (
```

```
    MW => MW,
```

```
    MM => MM,
```

```
    RW => RW,
```

```
    MD => MD,
```

```
    FS => FS,
```

```
    MB => MB,
```

```
    TB => TB,
```

```
    TA => TA,
```

```
    TD => TD,
```

```
    PL => PL,
```

```
    PI => PI,
```

```
    IL => IL,
```

```
    MC => MC,
```

```
    MS => MS,
```

```
    NA => NA,
```

```
    IN_CAR => IN_CAR
```

```
);
```

```
-- Stimulus process
```

```
stim_proc0: process
```

```
begin
```

```
    --Test that accessing IF address gives out the IF code:
```

```
    -- Next Address  MS          MC IL  PI      PL      TD TA  TB      MB      FS
MDRW  MM    MW
```

```

0      --      C1      001  0    1    1    0    0
0      0      0      00000 0    0    1    0

    IN_CAR <= x"C0";

    wait for 100 ns;

    --Test that accessing B address gives out the B code:

    -- Next Address  MS      MC IL  PI      PL      TD TA  TB      MB      FS
MDRW  MM      MW
0      --      C0      001  0    0    0    0    0    1    0
0      0      0      00000 0    0    0    0

    IN_CAR <= x"30";

    wait;

end process;

```

```
END;
```

3.10 ARITHMETIC CIRCUIT

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY arithmetic_circuit_16bit_TestBench IS
```

```
END arithmetic_circuit_16bit_TestBench;
```

```
ARCHITECTURE behavior OF arithmetic_circuit_16bit_TestBench IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT arithmetic_circuit_16bit
```

```
PORT(
```

```
    Cin : IN std_logic;
```

```

    S0 : IN std_logic;
    S1 : IN std_logic;
    A : IN std_logic_vector(15 downto 0);
    B : IN std_logic_vector(15 downto 0);
    G : OUT std_logic_vector(15 downto 0);
    Cout : OUT std_logic;
        Vout : OUT std_logic
    );
END COMPONENT;

```

--Inputs

```

signal Cin : std_logic := '0';
signal S0 : std_logic := '0';
signal S1 : std_logic := '0';
signal A : std_logic_vector(15 downto 0) := (others => '0');
signal B : std_logic_vector(15 downto 0) := (others => '0');

```

--Outputs

```

signal G : std_logic_vector(15 downto 0);
signal Cout : std_logic;
signal Vout : std_logic;
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name

```

BEGIN

```

    -- Instantiate the Unit Under Test (UUT)
    uut: arithmetic_circuit_16bit PORT MAP (

```

```

Cin => Cin,
S0 => S0,
S1 => S1,
A => A,
B => B,
G => G,
Cout => Cout,
        Vout => Vout
);

```

-- Stimulus process

stim_proc0: process

begin

wait for 100 ns;

Cin <= '0';

S0 <= '0';

S1 <= '0';

A <= x"000A";

B <= x"0000";

--Should place 0xA000 into G

wait for 100 ns;

S0 <= '0';

S1 <= '0';

Cin <= '1';

A <= x"000A";

B <= x"0000";

--Should place 0xA000 + 1 into G


```
wait for 100 ns;  
S0 <= '0';  
S1 <= '1';  
Cin <= '0';  
A <= x"000A";  
B <= x"FFF1";  
--Should place 0xA000 + ~(0xFFF1) into G
```

```
wait for 100 ns;  
S0 <= '0';  
S1 <= '1';  
Cin <= '1';  
A <= x"000A";  
B <= x"FFF1";  
--Should place 0xA000 + ~(0xFFF1) + 1 into G
```

```
wait for 100 ns;  
S0 <= '1';  
S1 <= '0';  
Cin <= '0';  
A <= x"000A";  
B <= x"00A0";  
--Should place 0xA000 + 0x00A0 into G
```

```
wait for 100 ns;  
S0 <= '1';  
S1 <= '0';  
Cin <= '1';  
A <= x"000A";
```

```
B <= x"00A0";  
--Should place 0xA000 + 0x00A0 + 1 into G
```

```
wait for 100 ns;  
S0 <= '1';  
S1 <= '1';  
Cin <= '0';  
A <= x"000A";  
B <= x"FFFF";  
--Should place 0xA000 - 1 into G
```

```
wait for 100 ns;  
S0 <= '1';  
S1 <= '1';  
Cin <= '1';  
A <= x"000A";  
B <= x"FFFF";  
--Should place 0xA000 G
```

```
end process;
```

```
END;
```

3.11 FUNCTIONAL UNIT

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY functional_unit_16bit_TestBench IS
```

```
END functional_unit_16bit_TestBench;
```

```
ARCHITECTURE behavior OF functional_unit_16bit_TestBench IS
```

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT functional_unit_16bit

PORT(

 FSS : IN std_logic_vector(4 downto 0);

 A : IN std_logic_vector(15 downto 0);

 B : IN std_logic_vector(15 downto 0);

 F : OUT std_logic_vector(15 downto 0);

 V : OUT std_logic;

 C : OUT std_logic;

 N : OUT std_logic;

 Z : OUT std_logic

);

END COMPONENT;

--Inputs

signal FSS : std_logic_vector(4 downto 0) := (others => '0');

signal A : std_logic_vector(15 downto 0) := (others => '0');

signal B : std_logic_vector(15 downto 0) := (others => '0');

--Outputs

signal F : std_logic_vector(15 downto 0);

signal V : std_logic;

signal C : std_logic;

signal N : std_logic;

signal Z : std_logic;

-- No clocks detected in port list. Replace <clock> below with

-- appropriate port name

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: functional_unit_16bit PORT MAP (

FSS => FSS,

A => A,

B => B,

F => F,

V => V,

C => C,

N => N,

Z => Z

);

--CYCLE THROUGH INPUTS TO TEST

-- EACH OPERATION

stim_proc1: process

begin

wait for 50 ns;

FSS(0) <= not FSS(0);

end process;

stim_proc2: process

begin

wait for 100 ns;

FSS(1) <= not FSS(1);

```
end process;
```

```
stim_proc3: process
```

```
begin
```

```
    wait for 200 ns;
```

```
        FSS(2) <= not FSS(2);
```

```
end process;
```

```
stim_proc4: process
```

```
begin
```

```
    wait for 400 ns;
```

```
        FSS(3) <= not FSS(3);
```

```
end process;
```

```
stim_proc5: process
```

```
begin
```

```
    wait for 800 ns;
```

```
        FSS(4) <= not FSS(4);
```

```
end process;
```

```
stim_proc6: process
```

```
begin
```

```
    A <= x"00FA";
```

```
    B <= x"002A";
```

```
    wait;
```

```
end process;
```

```
END;
```

3.12 MEMORY

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```

```
--USE ieee.numeric_std.ALL;
```

```
ENTITY memory_512_TestBench IS
```

```
END memory_512_TestBench;
```

```
ARCHITECTURE behavior OF memory_512_TestBench IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT memory_512
```

```
PORT(
```

```
    address : IN std_logic_vector(15 downto 0);
```

```
    write_data : IN std_logic_vector(15 downto 0);
```

```
    MemWrite : IN std_logic;
```

```
    read_data : OUT std_logic_vector(15 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal address : std_logic_vector(15 downto 0) := (others => '0');
```

```
signal write_data : std_logic_vector(15 downto 0) := (others => '0');
```

```
signal MemWrite : std_logic := '0';
```

```

        --Outputs
signal read_data : std_logic_vector(15 downto 0);

BEGIN

        -- Instantiate the Unit Under Test (UUT)
uut: memory_512 PORT MAP (
        address => address,
        write_data => write_data,
        MemWrite => MemWrite,
        read_data => read_data
    );

    -- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;

        write_data <= x"8003";
        address <= x"0002";
        MemWrite <= '1';

    wait for 100 ns;

    wait;
end process;

END;

```

3.13 ZERO-FILL

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY zero_fill_TestBench IS
```

```
END zero_fill_TestBench;
```

```
ARCHITECTURE behavior OF zero_fill_TestBench IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT zero_fill
```

```
PORT(
```

```
    SB : IN  std_logic_vector(2 downto 0);
```

```
    constant_out : OUT std_logic_vector(15 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal SB : std_logic_vector(2 downto 0) := (others => '0');
```

```
--Outputs
```

```
signal constant_out : std_logic_vector(15 downto 0);
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: zero_fill PORT MAP (
```



```

        SB => SB,
        constant_out => constant_out
    );

-- Stimulus process
stim_proc: process
begin
    --Test with the constant as 5
    SB <= "101";
    wait for 100 ns;

    --Test with the constant as 0
    SB <= "000";
    wait for 100 ns;

    --Test with the constant as 2
    SB <= "010";
    wait;
end process;

END;
```

3.14 RIPPLE ADDER

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY ripple_adder_16bit_TestBench IS
END ripple_adder_16bit_TestBench;

ARCHITECTURE behavior OF ripple_adder_16bit_TestBench IS
```

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT ripple_adder_16bit

PORT(

 A : IN std_logic_vector(15 downto 0);

 B : IN std_logic_vector(15 downto 0);

 Cin : IN std_logic;

 Cout : OUT std_logic;

 Vout : OUT std_logic;

 S : OUT std_logic_vector(15 downto 0)

);

END COMPONENT;

--Inputs

signal A : std_logic_vector(15 downto 0) := (others => '0');

signal B : std_logic_vector(15 downto 0) := (others => '0');

signal Cin : std_logic := '0';

--Outputs

signal Cout : std_logic;

signal Vout : std_logic;

signal S : std_logic_vector(15 downto 0);

-- No clocks detected in port list. Replace <clock> below with

-- appropriate port name

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: ripple_adder_16bit PORT MAP (

A => A,

B => B,

Cin => Cin,

Cout => Cout,

Vout => Vout,

S => S

);

-- Stimulus process

stim_proc: process

begin

-- hold reset state for 100 ns.

wait for 100 ns;

-- $0 + 0 = 0$

A <= x"0000";

B <= x"0000";

Cin <= '0';

wait for 100 ns;

-- $2 + 2 = 4$

A <= x"0002";

B <= x"0002";

Cin <= '0';

wait for 100 ns;

-- $0 + 0 + 1 = 1$

```

        A <= x"0000";

        B <= x"0000";

        Cin <= '1';

wait for 100 ns;

        -- 65535 + 65535 = 0 (+ carry)

        A <= x"FFFF";

        B <= x"FFFF";

        Cin <= '0';

wait for 100 ns;

end process;
END;

```

3.15 REGISTER FILE

```

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY new_reg_file_9x16bit_TestBench IS
END new_reg_file_9x16bit_TestBench;

ARCHITECTURE behavior OF new_reg_file_9x16bit_TestBench IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT new_reg_file_9x16bit

```

```

PORT(
    des_sel : IN std_logic_vector(2 downto 0);
    a_sel : IN std_logic_vector(2 downto 0);
    b_sel : IN std_logic_vector(2 downto 0);

    TD : IN std_logic;
    TA : IN std_logic;
    TB : IN std_logic;

    load_enable : IN std_logic;
    reset : IN std_logic;
    Clk : IN std_logic;
    input_data : IN std_logic_vector(15 downto 0);
    a_data : OUT std_logic_vector(15 downto 0);
    b_data : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;

```

--Inputs

```

signal des_sel : std_logic_vector(2 downto 0) := (others => '0');
signal a_sel : std_logic_vector(2 downto 0) := (others => '0');
signal b_sel : std_logic_vector(2 downto 0) := (others => '0');
signal load_enable : std_logic := '0';
signal reset : std_logic := '0';
signal TD : std_logic := '0';
signal TA : std_logic := '0';
signal TB : std_logic := '0';
signal Clk : std_logic := '0';
signal input_data : std_logic_vector(15 downto 0) := (others => '0');

```

```

        --Outputs

signal a_data : std_logic_vector(15 downto 0);
signal b_data : std_logic_vector(15 downto 0);


-- Clock period definitions

constant Clk_period : time := 10 ns;


BEGIN


        -- Instantiate the Unit Under Test (UUT)
uut: new_reg_file_9x16bit PORT MAP (
    des_sel => des_sel,
    a_sel => a_sel,
    b_sel => b_sel,
    TD => TD,
    TA => TA,
    TB => TB,
    load_enable => load_enable,
    reset => reset,
    Clk => Clk,
    input_data => input_data,
    a_data => a_data,
    b_data => b_data
);


-- Clock process definitions

Clk_process :process
begin
    Clk <= '0';

```

```
        wait for Clk_period/2;
        Clk <= '1';
        wait for Clk_period/2;
end process;
```

```
-- Stimulus process
```

```
stim_proc: process
```

```
begin
```

```
    -- hold reset state for 100 ns.
```

```
        reset <= '1';
```

```
    wait for 100 ns;
```

```
        load_enable <= '1';
```

```
    --Load 0x0 into reg0
```

```
        input_data <= x"0000";
```

```
        des_sel(0) <= '0';
```

```
        des_sel(1) <= '0';
```

```
        des_sel(2) <= '0';
```

```
        TD <= '0';
```

```
    wait for Clk_period*10;
```

```
    --Load 0x1 into reg1
```

```
        input_data <= x"0001";
```

```
        des_sel(0) <= '1';
```

```
        des_sel(1) <= '0';
```

```
        des_sel(2) <= '0';
```

```
        TD <= '0';
```

wait for Clk_period*10;

--Load 0x2 into reg2

input_data <= x"0002";

des_sel(0) <= '0';

des_sel(1) <= '1';

des_sel(2) <= '0';

TD <= '0';

wait for Clk_period*10;

--Load 0x3 into reg3

input_data <= x"0003";

des_sel(0) <= '1';

des_sel(1) <= '1';

des_sel(2) <= '0';

TD <= '0';

wait for Clk_period*10;

--Load 0x4 into reg4

input_data <= x"0004";

des_sel(0) <= '0';

des_sel(1) <= '0';

des_sel(2) <= '1';

TD <= '0';

wait for Clk_period*10;

--Load 0x5 into reg5

input_data <= x"0005";

des_sel(0) <= '1';


```
des_sel(1) <= '0';  
des_sel(2) <= '1';  
TD <= '0';  
wait for Clk_period*10;
```

```
--Load 0x6 into reg6  
input_data <= x"0006";  
des_sel(0) <= '0';  
des_sel(1) <= '1';  
des_sel(2) <= '1';  
TD <= '0';  
wait for Clk_period*10;
```

```
--Load 0x7 into reg7  
input_data <= x"0007";  
des_sel(0) <= '1';  
des_sel(1) <= '1';  
des_sel(2) <= '1';  
TD <= '0';  
wait for Clk_period*10;
```

```
--Load 0x8 into reg8  
input_data <= x"0008";  
des_sel(0) <= '0';  
des_sel(1) <= '0';  
des_sel(2) <= '0';  
TD <= '1';  
wait for Clk_period*10;
```

```

        --Load reg3's value into a_data
        a_sel(0) <= '1';
        a_sel(1) <= '1';
        a_sel(2) <= '0';
        TA <= '0';

        --Load reg5's value into b_data
        b_sel(0) <= '1';
        b_sel(1) <= '0';
        b_sel(2) <= '1';
        TB <= '0';
        wait;
    end process;
END;

```

3.16 LOGIC CIRCUIT

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY logic_circuit_16bit_TestBench IS
END logic_circuit_16bit_TestBench;

ARCHITECTURE behavior OF logic_circuit_16bit_TestBench IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT logic_circuit_16bit
    PORT(
        A : IN std_logic_vector(15 downto 0);

```

```

    B : IN std_logic_vector(15 downto 0);
    s0 : IN std_logic;
    s1 : IN std_logic;
    Y : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;

```

--Inputs

```

signal A : std_logic_vector(15 downto 0) := (others => '0');
signal B : std_logic_vector(15 downto 0) := (others => '0');
signal s0 : std_logic := '0';
signal s1 : std_logic := '0';

```

--Outputs

```

signal Y : std_logic_vector(15 downto 0);
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name

```

BEGIN

-- Instantiate the Unit Under Test (UUT)

```

uut: logic_circuit_16bit PORT MAP (
    A => A,
    B => B,
    s0 => s0,
    s1 => s1,
    Y => Y
);

```

```

-- Stimulus process
stim_proc0: process
begin
    wait for 25 ns;
        S0 <= not S0;
end process;

stim_proc1: process
begin
    wait for 50 ns;
        S1 <= not S1;
end process;

stim_proc2: process
begin
    A <= x"00A0";
    B <= x"002A";

    wait for 100 ns;
end process;
END;

```

3.17 DATAPATH

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

```

```
ENTITY last_data_path_TestBench IS
```

```
END last_data_path_TestBench;
```

```
ARCHITECTURE behavior OF last_data_path_TestBench IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT last_data_path
```

```
PORT(
```

```
    PC : IN  std_logic_vector(15 downto 0);
```

```
    data_in : IN  std_logic_vector(15 downto 0);
```

```
    DR : IN  std_logic_vector(2 downto 0);
```

```
    SA : IN  std_logic_vector(2 downto 0);
```

```
    SB : IN  std_logic_vector(2 downto 0);
```

```
    TD : IN  std_logic;
```

```
    TA : IN  std_logic;
```

```
    TB : IN  std_logic;
```

```
    Clk : IN  std_logic;
```

```
        reset : out std_logic;
```

```
    FS : IN  std_logic_vector(4 downto 0);
```

```
    RW : IN  std_logic;
```

```
    MB : IN  std_logic;
```

```
    MM : IN  std_logic;
```

```
    MD : IN  std_logic;
```

```
    data_out : OUT  std_logic_vector(15 downto 0);
```

```
    address_out : OUT  std_logic_vector(15 downto 0);
```

```
    V : OUT  std_logic;
```

```
    C : OUT  std_logic;
```

```
    N : OUT  std_logic;
```

```
    Z : OUT std_logic
);
END COMPONENT;
```

--Inputs

```
signal PC : std_logic_vector(15 downto 0) := (others => '0');
signal data_in : std_logic_vector(15 downto 0) := (others => '0');
signal DR : std_logic_vector(2 downto 0) := (others => '0');
signal SA : std_logic_vector(2 downto 0) := (others => '0');
signal SB : std_logic_vector(2 downto 0) := (others => '0');
signal TD : std_logic := '0';
signal TA : std_logic := '0';
signal TB : std_logic := '0';
signal Clk : std_logic := '0';
signal reset : std_logic := '0';
signal FS : std_logic_vector(4 downto 0) := (others => '0');
signal RW : std_logic := '0';
signal MB : std_logic := '0';
signal MM : std_logic := '0';
signal MD : std_logic := '0';
```

--Outputs

```
signal data_out : std_logic_vector(15 downto 0);
signal address_out : std_logic_vector(15 downto 0);
signal V : std_logic;
signal C : std_logic;
signal N : std_logic;
signal Z : std_logic;
```

-- Clock period definitions

constant Clk_period : time := 10 ns;

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: last_data_path PORT MAP (

PC => PC,

data_in => data_in,

DR => DR,

SA => SA,

SB => SB,

TD => TD,

TA => TA,

TB => TB,

Clk => Clk,

reset => reset,

FS => FS,

RW => RW,

MB => MB,

MM => MM,

MD => MD,

data_out => data_out,

address_out => address_out,

V => V,

C => C,

N => N,

Z => Z

```
);
```

```
-- Clock process definitions
```

```
Clk_process :process
```

```
begin
```

```
    Clk <= '0';
```

```
    wait for Clk_period/2;
```

```
    Clk <= '1';
```

```
    wait for Clk_period/2;
```

```
end process;
```

```
-- Stimulus process
```

```
stim_proc: process
```

```
begin
```

```
    -- hold reset state for 100 ns.
```

```
    wait for 100 ns;
```

```
    wait for Clk_period*10;
```

```
    -- insert stimulus here
```

```
    wait;
```

```
end process;
```

```
END;
```

3.18 DECODER3_8

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```



```
ENTITY decoder_3to8_TestBench IS
```

```
END decoder_3to8_TestBench;
```

```
ARCHITECTURE behavior OF decoder_3to8_TestBench IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT decoder_3to8
```

```
PORT(
```

```
    A0 : IN std_logic;
```

```
    A1 : IN std_logic;
```

```
    A2 : IN std_logic;
```

```
    Q0 : OUT std_logic;
```

```
    Q1 : OUT std_logic;
```

```
    Q2 : OUT std_logic;
```

```
    Q3 : OUT std_logic;
```

```
    Q4 : OUT std_logic;
```

```
    Q5 : OUT std_logic;
```

```
    Q6 : OUT std_logic;
```

```
    Q7 : OUT std_logic;
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal A0 : std_logic := '0';
```

```
signal A1 : std_logic := '0';
```

```
signal A2 : std_logic := '0';
```

--Outputs

signal Q0 : std_logic;

signal Q1 : std_logic;

signal Q2 : std_logic;

signal Q3 : std_logic;

signal Q4 : std_logic;

signal Q5 : std_logic;

signal Q6 : std_logic;

signal Q7 : std_logic;

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: decoder_3to8 PORT MAP (

A0 => A0,

A1 => A1,

A2 => A2,

Q0 => Q0,

Q1 => Q1,

Q2 => Q2,

Q3 => Q3,

Q4 => Q4,

Q5 => Q5,

Q6 => Q6,

Q7 => Q7

);

-- Stimulus process

stim_proc0: process

```

begin
    wait for 100 ns;
        A2 <= not A2;
end process;

stim_proc1: process
begin
    wait for 50 ns;
        A1 <= not A1;
end process;

stim_proc2: process
begin
    wait for 25 ns;
        A0 <= not A0;
end process;
END;

```

3.19 DECODER4_16

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

```

```

ENTITY decoder_4to16_TestBench IS
END decoder_4to16_TestBench;

```

```

ARCHITECTURE behavior OF decoder_4to16_TestBench IS

```

```

    -- Component Declaration for the Unit Under Test (UUT)

```

```

    COMPONENT decoder_4to16

```

```
PORT(  
    A0 : IN std_logic;  
    A1 : IN std_logic;  
    A2 : IN std_logic;  
    A3 : IN std_logic;  
    Q0 : OUT std_logic;  
    Q1 : OUT std_logic;  
    Q2 : OUT std_logic;  
    Q3 : OUT std_logic;  
    Q4 : OUT std_logic;  
    Q5 : OUT std_logic;  
    Q6 : OUT std_logic;  
    Q7 : OUT std_logic;  
    Q8 : OUT std_logic;  
    Q9 : OUT std_logic;  
    Q10 : OUT std_logic;  
    Q11 : OUT std_logic;  
    Q12 : OUT std_logic;  
    Q13 : OUT std_logic;  
    Q14 : OUT std_logic;  
    Q15 : OUT std_logic  
);  
END COMPONENT;
```

--Inputs

```
signal A0 : std_logic := '0';  
signal A1 : std_logic := '0';  
signal A2 : std_logic := '0';
```

```
signal A3 : std_logic := '0';
```

```
--Outputs
```

```
signal Q0 : std_logic;
```

```
signal Q1 : std_logic;
```

```
signal Q2 : std_logic;
```

```
signal Q3 : std_logic;
```

```
signal Q4 : std_logic;
```

```
signal Q5 : std_logic;
```

```
signal Q6 : std_logic;
```

```
signal Q7 : std_logic;
```

```
signal Q8 : std_logic;
```

```
signal Q9 : std_logic;
```

```
signal Q10 : std_logic;
```

```
signal Q11 : std_logic;
```

```
signal Q12 : std_logic;
```

```
signal Q13 : std_logic;
```

```
signal Q14 : std_logic;
```

```
signal Q15 : std_logic;
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: decoder_4to16 PORT MAP (
```

```
    A0 => A0,
```

```
    A1 => A1,
```

```
    A2 => A2,
```

```
    A3 => A3,
```

```
    Q0 => Q0,
```

```
Q1 => Q1,  
Q2 => Q2,  
Q3 => Q3,  
Q4 => Q4,  
Q5 => Q5,  
Q6 => Q6,  
Q7 => Q7,  
Q8 => Q8,  
Q9 => Q9,  
Q10 => Q10,  
Q11 => Q11,  
Q12 => Q12,  
Q13 => Q13,  
Q14 => Q14,  
Q15 => Q15  
);
```

-- Stimulus process

```
stim_proc3: process  
begin  
    wait for 200 ns;  
    A3 <= not A3;  
end process;
```

```
stim_proc0: process  
begin  
    wait for 100 ns;  
    A2 <= not A2;
```

```
end process;
```

```
stim_proc1: process
```

```
begin
```

```
    wait for 50 ns;
```

```
        A1 <= not A1;
```

```
end process;
```

```
stim_proc2: process
```

```
begin
```

```
    wait for 25 ns;
```

```
        A0 <= not A0;
```

```
end process;
```

```
END;
```

3.20 MUX16_16BIT

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY mux16_16bit_TestBench IS
```

```
END mux16_16bit_TestBench;
```

```
ARCHITECTURE behavior OF mux16_16bit_TestBench IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT mux16_16bit
```

```
PORT(
```

```
    S0 : IN std_logic;
```

```

S1 : IN std_logic;
S2 : IN std_logic;
S3 : IN std_logic;

In0 : IN std_logic_vector(15 downto 0);
In1 : IN std_logic_vector(15 downto 0);
In2 : IN std_logic_vector(15 downto 0);
In3 : IN std_logic_vector(15 downto 0);
In4 : IN std_logic_vector(15 downto 0);
In5 : IN std_logic_vector(15 downto 0);
In6 : IN std_logic_vector(15 downto 0);
In7 : IN std_logic_vector(15 downto 0);
In8 : IN std_logic_vector(15 downto 0);
In9 : IN std_logic_vector(15 downto 0);
In10 : IN std_logic_vector(15 downto 0);
In11 : IN std_logic_vector(15 downto 0);
In12 : IN std_logic_vector(15 downto 0);
In13 : IN std_logic_vector(15 downto 0);
In14 : IN std_logic_vector(15 downto 0);
In15 : IN std_logic_vector(15 downto 0);
Z : OUT std_logic_vector(15 downto 0)
);

END COMPONENT;

```

--Inputs

```

signal S0 : std_logic := '0';
signal S1 : std_logic := '0';
signal S2 : std_logic := '0';
signal S3 : std_logic := '0';

```



```

signal In0 : std_logic_vector(15 downto 0) := (others => '0');
signal In1 : std_logic_vector(15 downto 0) := (others => '0');
signal In2 : std_logic_vector(15 downto 0) := (others => '0');
signal In3 : std_logic_vector(15 downto 0) := (others => '0');
signal In4 : std_logic_vector(15 downto 0) := (others => '0');
signal In5 : std_logic_vector(15 downto 0) := (others => '0');
signal In6 : std_logic_vector(15 downto 0) := (others => '0');
signal In7 : std_logic_vector(15 downto 0) := (others => '0');
signal In8 : std_logic_vector(15 downto 0) := (others => '0');
signal In9 : std_logic_vector(15 downto 0) := (others => '0');
signal In10 : std_logic_vector(15 downto 0) := (others => '0');
signal In11 : std_logic_vector(15 downto 0) := (others => '0');
signal In12 : std_logic_vector(15 downto 0) := (others => '0');
signal In13 : std_logic_vector(15 downto 0) := (others => '0');
signal In14 : std_logic_vector(15 downto 0) := (others => '0');
signal In15 : std_logic_vector(15 downto 0) := (others => '0');

```

--Outputs

```

signal Z : std_logic_vector(15 downto 0);

```

BEGIN

-- Instantiate the Unit Under Test (UUT)

```

uut: mux16_16bit PORT MAP (

```

```

    S0 => S0,
```

```

    S1 => S1,
```

```

    S2 => S2,
```

```

    S3 => S3,
```

```

    In0 => In0,
```

```
ln1 => ln1,  
ln2 => ln2,  
ln3 => ln3,  
ln4 => ln4,  
ln5 => ln5,  
ln6 => ln6,  
ln7 => ln7,  
ln8 => ln8,  
ln9 => ln9,  
ln10 => ln10,  
ln11 => ln11,  
ln12 => ln12,  
ln13 => ln13,  
ln14 => ln14,  
ln15 => ln15,  
Z => Z  
);
```

```
-- Stimulus process
```

```
stim_proc4: process
```

```
begin
```

```
    wait for 200 ns;
```

```
        S3 <= not S3;
```

```
end process;
```

```
stim_proc0: process
```

```
begin
```

```
    wait for 100 ns;
```

```
        S2 <= not S2;
```

```
end process;
```

```
stim_proc1: process
```

```
begin
```

```
    wait for 50 ns;
```

```
        S1 <= not S1;
```

```
end process;
```

```
stim_proc2: process
```

```
begin
```

```
    wait for 25 ns;
```

```
        S0 <= not S0;
```

```
end process;
```

```
stim_proc3: process
```

```
begin
```

```
    In0 <= x"0000";
```

```
    In1 <= x"0001";
```

```
    In2 <= x"0002";
```

```
    In3 <= x"0003";
```

```
    In4 <= x"0004";
```

```
    In5 <= x"0005";
```

```
    In6 <= x"0006";
```

```
    In7 <= x"0007";
```

```
    In8 <= x"0008";
```

```
    In9 <= x"0009";
```

```
    In10 <= x"000A";
```

```
    In11 <= x"000B";
```

```
    In12 <= x"000C";
```

```

        ln13 <= x"000D";
        ln14 <= x"000E";
        ln15 <= x"000F";
        wait;
    end process;

```

```
END;
```

3.21 MUX16_1BIT

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY mux16_1bit_TestBench IS
```

```
END mux16_1bit_TestBench;
```

```
ARCHITECTURE behavior OF mux16_1bit_TestBench IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT mux16_1bit
```

```
PORT(
```

```
    S0 : IN std_logic;
```

```
    S1 : IN std_logic;
```

```
    S2 : IN std_logic;
```

```
    S3 : IN std_logic;
```

```
    A : IN std_logic_vector(15 downto 0);
```

```
    F : OUT std_logic
```

```
);
```

```
END COMPONENT;
```

--Inputs

signal S0 : std_logic := '0';

signal S1 : std_logic := '0';

signal S2 : std_logic := '0';

signal S3 : std_logic := '0';

signal A : std_logic_vector(15 downto 0) := (others => '0');

--Outputs

signal F : std_logic;

-- No clocks detected in port list. Replace <clock> below with

-- appropriate port name

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: mux16_1bit PORT MAP (

S0 => S0,

S1 => S1,

S2 => S2,

S3 => S3,

A => A,

F => F

);

-- Stimulus process

stim_proc0: process

```

begin
    wait for 25 ns;
        S0 <= not S0;
end process;

stim_proc1: process
begin
    wait for 50 ns;
        S1 <= not S1;
end process;

stim_proc2: process
begin
    wait for 100 ns;
        S2 <= not S2;
end process;

    stim_proc3: process
begin
    wait for 200 ns;
        S3 <= not S3;
end process;

    stim_proc4: process
begin
        A <= x"AAAA";

        wait for 400 ns;
end process;

END;

```

3.22 MUX2_16BIT

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

ENTITY mux_2_16bit_TestBench IS

END mux_2_16bit_TestBench;

ARCHITECTURE behavior OF mux_2_16bit_TestBench IS

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT mux_2_16bit

PORT(

S : IN std_logic;

In0 : IN std_logic_vector(15 downto 0);

In1 : IN std_logic_vector(15 downto 0);

Z : OUT std_logic_vector(15 downto 0)

);

END COMPONENT;

--Inputs

signal S : std_logic := '0';

signal In0 : std_logic_vector(15 downto 0) := (others => '0');

signal In1 : std_logic_vector(15 downto 0) := (others => '0');

--Outputs

signal Z : std_logic_vector(15 downto 0);

BEGIN

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: mux_2_16bit PORT MAP (
```

```
    S => S,
```

```
    In0 => In0,
```

```
    In1 => In1,
```

```
    Z => Z
```

```
);
```

```
-- Stimulus process
```

```
stim_proc0: process
```

```
begin
```

```
    In0 <= x"AAAA";
```

```
        In1 <= x"FFFF";
```

```
        wait for 300 ns;
```

```
end process;
```

```
-- Stimulus process
```

```
stim_proc1: process
```

```
begin
```

```
    wait for 100 ns;
```

```
        S <= not S;
```

```
end process;
```

```
END;
```

3.23 MUX2_8BIT

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```


-- arithmetic functions with Signed or Unsigned values

--USE ieee.numeric_std.ALL;

ENTITY mux_2_to_1_8bit_TestBench IS

END mux_2_to_1_8bit_TestBench;

ARCHITECTURE behavior OF mux_2_to_1_8bit_TestBench IS

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT mux_2_to_1_8bit

PORT(

In0 : IN std_logic_vector(7 downto 0);

In1 : IN std_logic_vector(7 downto 0);

S : IN std_logic;

Z : OUT std_logic_vector(7 downto 0)

);

END COMPONENT;

--Inputs

signal In0 : std_logic_vector(7 downto 0) := (others => '0');

signal In1 : std_logic_vector(7 downto 0) := (others => '0');

signal S : std_logic := '0';

--Outputs

signal Z : std_logic_vector(7 downto 0);

BEGIN

```

        -- Instantiate the Unit Under Test (UUT)
    uut: mux_2_to_1_8bit PORT MAP (
        In0 => In0,
        In1 => In1,
        S => S,
        Z => Z
    );

    -- Stimulus process
    stim_proc0: process
    begin
        In0 <= x"AA";
        In1 <= x"FF";
        wait for 300 ns;
    end process;

    -- Stimulus process
    stim_proc1: process
    begin
        wait for 100 ns;
        S <= not S;
    end process;
END;

```

3.24 MUX8_16BIT

```

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

ENTITY mux8_16bit_TestBench IS

```

```
END mux8_16bit_TestBench;
```

ARCHITECTURE behavior OF mux8_16bit_TestBench IS

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT mux8_16bit
```

```
PORT(
```

```
    S0 : IN  std_logic;
```

```
    S1 : IN  std_logic;
```

```
    S2 : IN  std_logic;
```

```
    In0 : IN  std_logic_vector(15 downto 0);
```

```
    In1 : IN  std_logic_vector(15 downto 0);
```

```
    In2 : IN  std_logic_vector(15 downto 0);
```

```
    In3 : IN  std_logic_vector(15 downto 0);
```

```
    In4 : IN  std_logic_vector(15 downto 0);
```

```
    In5 : IN  std_logic_vector(15 downto 0);
```

```
    In6 : IN  std_logic_vector(15 downto 0);
```

```
    In7 : IN  std_logic_vector(15 downto 0);
```

```
    Z : OUT  std_logic_vector(15 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal S0 : std_logic := '0';
```

```
signal S1 : std_logic := '0';
```

```
signal S2 : std_logic := '0';
```

```
signal In0 : std_logic_vector(15 downto 0) := (others => '0');
```

```
signal In1 : std_logic_vector(15 downto 0) := (others => '0');
```

```
signal In2 : std_logic_vector(15 downto 0) := (others => '0');
signal In3 : std_logic_vector(15 downto 0) := (others => '0');
signal In4 : std_logic_vector(15 downto 0) := (others => '0');
signal In5 : std_logic_vector(15 downto 0) := (others => '0');
signal In6 : std_logic_vector(15 downto 0) := (others => '0');
signal In7 : std_logic_vector(15 downto 0) := (others => '0');
```

--Outputs

```
signal Z : std_logic_vector(15 downto 0);
```

BEGIN

-- Instantiate the Unit Under Test (UUT)

```
uut: mux8_16bit PORT MAP (
```

```
    S0 => S0,
```

```
    S1 => S1,
```

```
    S2 => S2,
```

```
    In0 => In0,
```

```
    In1 => In1,
```

```
    In2 => In2,
```

```
    In3 => In3,
```

```
    In4 => In4,
```

```
    In5 => In5,
```

```
    In6 => In6,
```

```
    In7 => In7,
```

```
    Z => Z
```

```
);
```

-- Stimulus process

```
stim_proc0: process
```

```
begin
```

```
    wait for 100 ns;
```

```
        S2 <= not S2;
```

```
end process;
```

```
stim_proc1: process
```

```
begin
```

```
    wait for 50 ns;
```

```
        S1 <= not S1;
```

```
end process;
```

```
stim_proc2: process
```

```
begin
```

```
    wait for 25 ns;
```

```
        S0 <= not S0;
```

```
end process;
```

```
stim_proc3: process
```

```
begin
```

```
    In0 <= x"0000";
```

```
    In1 <= x"0001";
```

```
    In2 <= x"0002";
```

```
    In3 <= x"0003";
```

```
    In4 <= x"0004";
```

```
    In5 <= x"0005";
```

```
    In6 <= x"0006";
```

```
    In7 <= x"0007";
```

```
    wait for 200 ns;
```

```
end process;
```

```
END;
```

3.25 MUX8_1BIT

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY mux_8_to_1_1bit_TestBench IS
```

```
END mux_8_to_1_1bit_TestBench;
```

```
ARCHITECTURE behavior OF mux_8_to_1_1bit_TestBench IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT mux_8_to_1_1bit
```

```
PORT(
```

```
    A : IN std_logic_vector(7 downto 0);
```

```
    S0 : IN std_logic;
```

```
    S1 : IN std_logic;
```

```
    S2 : IN std_logic;
```

```
    line_out : OUT std_logic
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal A : std_logic_vector(7 downto 0) := (others => '0');
```

```
signal S0 : std_logic := '0';
```

```
signal S1 : std_logic := '0';
```

```
signal S2 : std_logic := '0';
```

```
--Outputs
```

```
signal line_out : std_logic;
```

```
-- No clocks detected in port list. Replace <clock> below with
```

```
-- appropriate port name
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: mux_8_to_1_1bit PORT MAP (
```

```
    A => A,
```

```
    S0 => S0,
```

```
    S1 => S1,
```

```
    S2 => S2,
```

```
    line_out => line_out
```

```
);
```

```
stim_proc0: process
```

```
begin
```

```
    wait for 25 ns;
```

```
        S0 <= not S0;
```

```
end process;
```

```
stim_proc1: process
```

```
begin
```

```
    wait for 50 ns;
```

```
        S1 <= not S1;
```

```

end process;

stim_proc2: process
begin
    wait for 100 ns;
        S2 <= not S2;
end process;

```

```

        stim_proc4: process
begin
        A <= x"AA";

    wait for 400 ns;
end process;

```

```

END;

```

3.26 FULL ADDER

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

```

```

ENTITY full_adder_TestBench IS
END full_adder_TestBench;

```

```

ARCHITECTURE behavior OF full_adder_TestBench IS

```

```

    -- Component Declaration for the Unit Under Test (UUT)

```

```

    COMPONENT full_adder

```

```

    PORT(

```

```

        A : IN std_logic;

```



```
B : IN std_logic;  
Cin : IN std_logic;  
S : OUT std_logic;  
Cout : OUT std_logic  
);  
END COMPONENT;
```

--Inputs

```
signal A : std_logic := '0';  
signal B : std_logic := '0';  
signal Cin : std_logic := '0';
```

--Outputs

```
signal S : std_logic;  
signal Cout : std_logic;
```

BEGIN

-- Instantiate the Unit Under Test (UUT)

```
uut: full_adder PORT MAP (  
    A => A,  
    B => B,  
    Cin => Cin,  
    S => S,  
    Cout => Cout  
);
```

-- Stimulus process

```

stim_proc0: process
begin
    wait for 25 ns;

    Cin <= not Cin;
end process;

```

```

-- Stimulus process
stim_proc1: process
begin
    wait for 50 ns;

    B <= not B;
end process;

```

```

-- Stimulus process
stim_proc2: process
begin
    wait for 100 ns;

    A <= not A;
end process;

```

```

END;

```

3.27 MUXB_Y_16BIT

```

LIBRARY ieee;

```

```

USE ieee.std_logic_1164.ALL;

```

```

ENTITY b_to_y_16bit_TestBench IS

```

```

END b_to_y_16bit_TestBench;

```

```

ARCHITECTURE behavior OF b_to_y_16bit_TestBench IS

```

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT b_to_y_16bit

PORT(

 B : IN std_logic_vector(15 downto 0);

 Y : OUT std_logic_vector(15 downto 0);

 S0 : IN std_logic;

 S1 : IN std_logic

);

END COMPONENT;

--Inputs

signal B : std_logic_vector(15 downto 0) := (others => '0');

signal S0 : std_logic := '0';

signal S1 : std_logic := '0';

--Outputs

signal Y : std_logic_vector(15 downto 0);

-- No clocks detected in port list. Replace <clock> below with

-- appropriate port name

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: b_to_y_16bit PORT MAP (

 B => B,

 Y => Y,

```

        S0 => S0,
        S1 => S1
    );
    -- Stimulus process

stim_proc0: process
begin
    wait for 100 ns;
    B <= x"AAAA";
end process;

stim_proc1: process
begin
    wait for 50 ns;
    S1 <= not S1;
end process;

stim_proc2: process
begin
    wait for 25 ns;
    S0 <= not S0;
end process;

END;
```

3.28 REGISTER

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY reg16_TestBench IS
```

```
END reg16_TestBench;
```

```
ARCHITECTURE behavior OF reg16_TestBench IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT reg16
```

```
PORT(
```

```
    D : IN  std_logic_vector(15 downto 0);
```

```
    load : IN  std_logic;
```

```
    Clk : IN  std_logic;
```

```
    Q : OUT  std_logic_vector(15 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal D : std_logic_vector(15 downto 0) := (others => '0');
```

```
signal load : std_logic := '0';
```

```
signal Clk : std_logic := '0';
```

```
--Outputs
```

```
signal Q : std_logic_vector(15 downto 0);
```

```
-- Clock period definitions
```

```
constant Clk_period : time := 10 ns;
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: reg16 PORT MAP (
```

```
    D => D,
```

```

    load => load,

    Clk => Clk,

    Q => Q

);

-- Clock process definitions

Clk_process :process
begin

    Clk <= '0';

    wait for Clk_period/2;

    Clk <= '1';

    wait for Clk_period/2;

end process;

-- Stimulus process

stim_proc0: process
begin

    wait for Clk_period*2;

    load <= '1';

    D <= x"AAAA";

    --Should load 0xAAAA into D

    wait for Clk_period*2;

    load <= '0';

    D <= x"1111";

    --Should not load 0x1111 into Q

    wait for Clk_period*2;

    load <= '1';

    D <= x"1111";

    --Should load 0x1111 into Q

```

end process;

END;